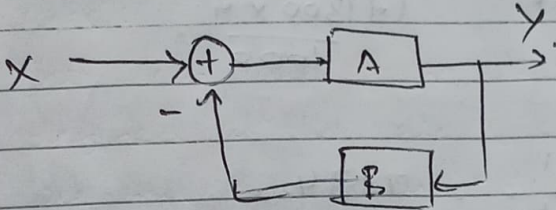


Assignment 5.

1. Given circuit:



$$A = 1000 \text{ V/V.}$$

$$\frac{A}{1+AK} = 100 \text{ V/V.}$$

i) Find the tolerance in closed loop gain if open loop tolerance is 30%.

\therefore for +30%.

$$A = 1300.$$

$$\frac{A}{1+AK} = \frac{1300}{1+1300 \times K} \quad \text{--- (1)}$$

$$1) K \leq 1/A$$

$$\frac{A}{1+AK} = 100.$$

$$2) \frac{1000}{1+AK} = 100$$

$$3) 1+AK = 10.$$

$$AK = 9.$$

$$K = \frac{9}{1000}$$

2) from (1)

$$\frac{A'}{1+A'K} = \frac{1300}{1 + \frac{1300 \times 9}{1000}}$$

$$\Rightarrow \frac{A'}{1+A'K} = 78.74.$$

for -30% .

$$\frac{700}{1 + \frac{9}{1000} \times 700} = 95.89\%$$

\therefore tolerance of closed loop = 21.26%

ii) if $A = 10$.

$$\Rightarrow \frac{1000}{1+1000K} = 10.$$

$$1+1000K = 100$$

$$1000K = 99$$

$$K = \frac{99}{1000}$$

$$\Rightarrow K = 0.099\%$$

$$\Rightarrow \frac{1300}{1 + \frac{1300 \times 99}{1000}} \quad \Rightarrow \quad \frac{1300}{13K} \quad \Rightarrow \quad 10.02\%$$

for $A = 700$.

$$\frac{700}{1 + 700 \times \frac{99}{1000}} \approx 9.95$$

$$\Rightarrow \text{tolerance} = \frac{10 - 9.95}{10}$$

$$\Rightarrow \boxed{0.005\%}$$

iii) When 2 stages are cascaded

$$g_{m1} = 10 \times 10 = 100 \text{ V/V} \quad \text{--- (1)}$$

tolerance

$$\Rightarrow 0.005 \times 0.005$$

$$= \cancel{0.0025} \quad \boxed{2.5 \times 10^{-5}} \% \quad \text{--- (2)}$$

2. Problem 7.2.

$$v_{n, \text{in}}^2 = 4KT \left(\frac{2}{3} \frac{1}{g_{m1}} + \frac{2}{3} \frac{g_{m2}}{g_{m1}^2} \right)$$

$$v_{n, \text{in}} = \sqrt{4KT \frac{2}{3}} \sqrt{\frac{1}{g_{m1}} + \frac{g_{m2}}{g_{m1}^2}}$$

$$\frac{g_{m2}}{g_{m1}^2} = \left(\frac{1}{5} \right)^2 \frac{1}{g_{m2}} \Rightarrow g_{m2} = \left(\frac{1}{5} \right)^2 g_{m1}$$

$$g_m = \frac{2I_D}{V_{GS} - V_T}$$

$$\Rightarrow V_{GS} - V_T = \frac{2I_D}{g_m}$$

$$\therefore \text{Output swing} = V_{DD} - (V_{GS1} - V_T) - [(V_{GS2} - V_T)]$$

$$= V_{DD} - 2I_D \left(\frac{1}{g_{m1}} + \frac{1}{g_{m2}} \right)$$

$$= V_{DD} - 2I_D \left(\frac{1}{g_{m1}} \right) (1+r^2)$$

$$g_{m1} = \sqrt{2I_D / \mu_n C_{ox} (W/L)} \approx 1.986 \text{ mA/V}$$

$$\therefore \text{output swing} = 3V - 2(1 \text{ mA}) \left(\frac{1}{1.986} \right) (26)$$

$$\Rightarrow \text{Output swing} = 0.38 \text{ V}$$

Problem 7.6:

$$a) |A_v| = \frac{g_m R_D}{1 + g_m R_S}$$

$$V_{n, \text{out}}^2 = 4KT R_D + 4KT \frac{2}{3} \frac{1}{g_m} \left(\frac{g_m R_D}{1 + g_m R_S} \right)^2$$

$$+ 4KT \frac{1}{R_S} \left(\frac{R_D}{1 + g_m R_S} \right)^2 R_D^2$$

$$= 4KT R_D + 4KT \frac{2}{3} \frac{1}{g_m} \left(\frac{g_m R_D}{1 + g_m R_S} \right)^2 + 4KT R_S$$

$$\left(\frac{g_m R_D}{1 + g_m R_S} \right)^2$$

$$v_{n, in}^2 = \frac{v_{n, out}^2}{|A_v|^2}$$

$$b) \quad |A_v| = g_m \left(\frac{1}{g_m} \parallel R_D \right)$$

$$v_{n, out}^2 = \left(4kT \frac{2}{3} g_m + 4kT \frac{1}{R_D} \right) \left(\frac{1}{g_m} \parallel R_D \right)^2$$

$$v_{n, in}^2 = \frac{v_{n, out}^2}{|A_v|^2}$$

$$= 4kT \frac{2}{3} \frac{1}{g_m} + 4kT \frac{1}{g_m^2 R_D}$$

$$c) \quad |A_v| = \frac{g_m}{1 + (g_m + \frac{1}{R_F}) R_D} \cdot R_{out}$$

$$R_{out} = R_D + (1 + g_m R_D) R_F$$

$$v_{n, out}^2 = \left(\frac{4kT \frac{2}{3} g_m}{(1 + (g_m + \frac{1}{R_F}) R_D)^2} + \frac{4kT \frac{1}{R_F}}{(1 + (g_m + \frac{1}{R_F}) R_D)^2} + \frac{4kT \frac{1}{R_D} R_D^2}{(R_D + \frac{1}{g_m} \parallel R_F)^2} \right) \times R_{out}^2$$

$$v_{n, in}^2 = 4kT \left(\frac{2}{3} \frac{1}{g_m} + \frac{1}{g_m^2 R_F} + R_D \left(1 + \frac{1}{g_m R_F} \right)^2 \right)$$

$$d) \quad |A_v| = \frac{g_{m1}}{1 + g_{m1} R_D} \times R_{out}$$

$$R_{out} = \frac{1}{g_{m2}}$$

$$V_{n,out}^2 = 4KT \frac{2}{3} g_{m2} R_{out}^2 + 4KT \frac{2}{3} \frac{1}{g_{m1}} |A_v|^2 +$$

$$4KT \frac{1}{R_D} \left(\frac{R_D}{1 + g_{m1} R_D} \right)^2 R_{out}^2$$

$$V_{n,out}^2 = 4KT \left[\frac{2}{3} \frac{1}{g_{m1}} + R_D + \frac{2}{3} g_{m2} \left(\frac{1 + g_{m1} R_D}{g_{m1}} \right)^2 \right]$$

e) $|A_v| = g_{m1} R_D$

$$V_{n,out}^2 = \left(4KT \frac{2}{3} g_{m1} + 4KT \frac{1}{R_D} \right) R_D^2$$

$$V_{n,out}^2 = 4KT \left(\frac{2}{3} \frac{1}{g_{m1}} + \frac{1}{g_{m1}^2 R_D} \right)$$

f) $|A_v| = g_{m1} \left(\frac{g_{m2} R_D}{1 + g_{m2} R_D} \right) R_D$

$$V_{n,out}^2 = \left[4KT \frac{1}{R_D} + 4KT \frac{2}{3} \frac{1}{g_{m2}} \left(\frac{g_{m2}}{1 + g_{m2} R_D} \right)^2 + 4KT \frac{2}{3} \frac{1}{g_{m1}} \left(\frac{g_{m2}}{1 + g_{m2} R_D} \right)^2 + 4KT \right] R_D^2$$

$$V_{n,out}^2 = 4KT \left[\frac{2}{3} g_{m1} + \frac{2}{3} \frac{1}{g_{m1}} \frac{1}{(g_{m1} R_D)^2} + \right.$$

$$\left. \frac{1}{g_{m1} R_D} + \frac{1}{g_{m1}^2 R_D} \left(\frac{1 + g_{m2} R_D}{g_{m1} R_D} \right)^2 \right]$$

3. Short note on non-linearity in diff. circuit.

It is used to measure performance
↳ DAC, ADC.

It refers to constant relation between
the change in output & input.

$$DNL(i) = \frac{V_{out}(i+1) - V_{out}(i)}{\text{ideal LSB step width}} - 1.$$

4. Problem 9.4.

$$\left(\frac{W}{L}\right)_{1.8} = \frac{100}{0.9}, \quad I_{SS} = 1 \text{ mA}, \quad V_{B1} = 1.7 \text{ V},$$

$$r = 0.$$

$$a) V_{in, common} = V_{iss} + V_{th}.$$

$$V_{OD3} = V_{B3} - V_{th} = \left[\frac{2103}{(4n \times 4/L)} \right]^{1/2}.$$

$$= \left(\frac{2103}{3.70 \times 383.6 \times 10^{-9} \times \frac{100}{0.9}} \right)^{1/2}.$$

$$= 0.179 \text{ V}$$

$$V_{in, CM, max} = 1.7 - 0.179 = 1.541 \text{ V}$$

$$b) V_x = ?$$

$$V_{out} - V_{thp} = \left[\frac{210\Omega}{h_{ie} h_{oe} \left(\frac{h_o}{L_{eff}} \right)} \right]^{1/2}$$

$$= 0.289$$

$$V_{out} = 0.289 + V_{thp} = 1.089 V$$

$$V_x = V_{DD} - V_{out} = 3 - 1.089$$

$$\boxed{V_x = 1.911 V}$$

$$c) V_{out} = V_{thp} = 0.159 V + V_{thp}$$

$$V_{out} = 0.7 + 0.159 = 0.859 V$$

$$\text{Max Swing} = 0.7 - 0.859 \text{ to } 0.2$$

$$\rightarrow \boxed{\text{Max Output Swing} = 0.541 V}$$

$$d) V_{b2} < V_x + V_{thp} - |V_{thp}| = 2.089 V$$

$$V_{b2} < 1.622 V$$

$$\boxed{1.011 V < V_{b2} < 1.62 V}$$

c) As M_3, M_4, M_5, M_6 have negligible noise

Input referred noise:

$$4kTR \left(\frac{1}{g_{m12}} + \frac{g_{m78}}{g_{m242}} \right) \times 2.$$

↳) ~~5024~~

$$= 5.45 \times 10^{-18} \text{ V}^2/\text{Hz}.$$

$$\boxed{\sqrt{N} = 2.34 \times 10^{-9} \text{ V}/\sqrt{\text{Hz}}}$$