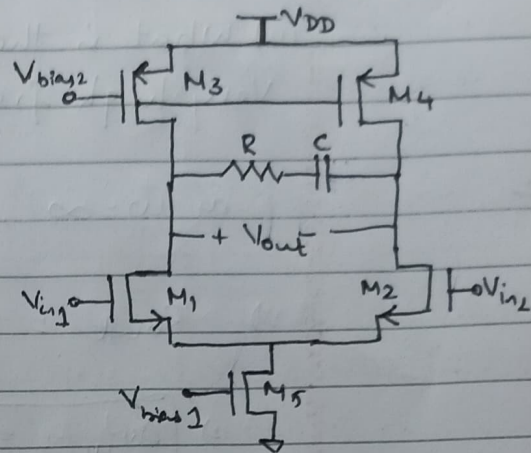


Assignment 3.

1. In the following circuit assume transistors M_1 and M_2 , and transistors M_3 and M_4 are identical and $r=0$, $\lambda \neq 0$.

- i) Find the expression for the small signal differential voltage gain ($V_{out}/V_{in1}-V_{in2}$) of the circuit.



Let impedance Z

$$= R + \frac{1}{j\omega C}$$

as Z is parallel to M_3 and to M_1 , when AC ground is applied,

R_{out} can be considered as $(r_{o1} || r_{o3} || \frac{Z}{2})$ on one side.

$$\Rightarrow R_{out} = (r_{o1} || r_{o3} || \frac{Z}{2})$$

$$\Rightarrow A_v = -g_{m1} (r_{o1} || r_{o3} || \frac{Z}{2})$$

- ii) What is the gain of the circuit is very low frequencies?

at low frequencies $\omega=0$.

$$\Rightarrow Z = R + \frac{1}{j\omega C} = R + \frac{1}{0} = \infty$$

a) $z = \infty$.

$$A_{V_{LF}} = -g_{m1} (r_{o1} \parallel r_{o3})$$

iii) What is the gain of the circuit at Very high frequencies?

a) $\omega = \infty$, $Z = R + \frac{1}{j\omega C} \rightarrow \frac{R + \frac{1}{\infty}}{\infty} = R$.

2) $R_{out} = r_{o1} \parallel r_{o3} \parallel R_{1/2}$.

$$2) A_{V_{HF}} = -g_{m1} (r_{o1} \parallel r_{o3} \parallel R_{1/2})$$

2. Assuming all transistors in saturation and ignoring CLM and body effect, Also, $(W/L)_3 = (W/L)_4$.

i) Find an expression for I_{out} .

$$\left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_4 \Rightarrow I_1 = I_3 = I_{out}$$


$$I_{out} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{DS2} - V_{th})^2$$

$$2) V_{DS2} = V_{thn} + \sqrt{\frac{2I_{out}}{\mu_n C_{ox} (W/L)_2}}$$

$$\text{Uy } V_{DS1} = V_{thn} + \sqrt{\frac{2I_{out}}{\mu_n C_{ox} (W/L)_1}}$$

Also,

$$V_{DS1} - V_{DS2} = I_{out} \times R$$

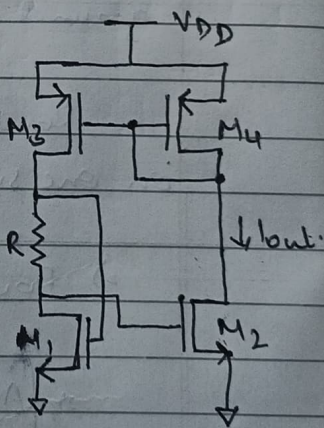

$$2) V_{th1} - V_{th2} = \left[V_{thn} + \sqrt{\frac{2I_{out}}{\mu_n \mu_{ox} (W/L)_1}} \right] - \left[V_{thn} - \sqrt{\frac{2I_{out}}{\mu_n \mu_{ox} (W/L)_2}} \right]$$

$$2) R I_{out} = \sqrt{\frac{2I_{out}}{\mu_n \mu_{ox}}} \left(\sqrt{\left(\frac{L}{W}\right)_1} - \sqrt{\frac{L}{W}_2} \right)$$

$$2) R \sqrt{I_{out}} = \sqrt{\frac{2}{\mu_n \mu_{ox}}} \left(\sqrt{\frac{L_1}{W_1}} - \sqrt{\frac{L_2}{W_2}} \right)$$

$$2) I_{out} = \frac{2}{\mu_n \mu_{ox} R^2} \left(\sqrt{\frac{L_1}{W_1}} - \sqrt{\frac{L_2}{W_2}} \right)^2$$


ii) What would be the percentage change in I_{out} if V_{DD} is increased by 10%.

As all transistors are in saturation, the I_{out} is independent of V_{DD} . Hence, there will be no change in I_{out} .

iii) How would the expression for I_{out} derived in part (i) change if $\Gamma \neq 0$ and why?


As $V_{SB1} = V_{SB2} = 0$, the resultant body effect would not change the I_{out} .

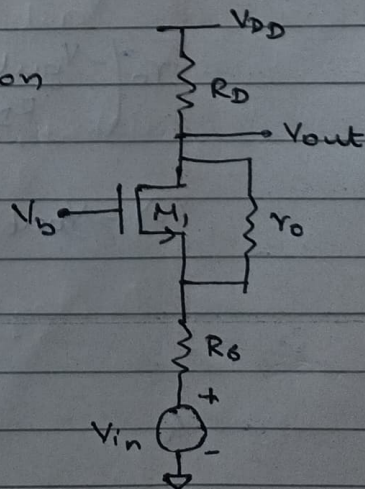3. Calculate the gain of the common gate amplifier as shown below considering both CLM and Body effect.



The current through R_S is same as $-V_{out} / R_D$.

Small signal:

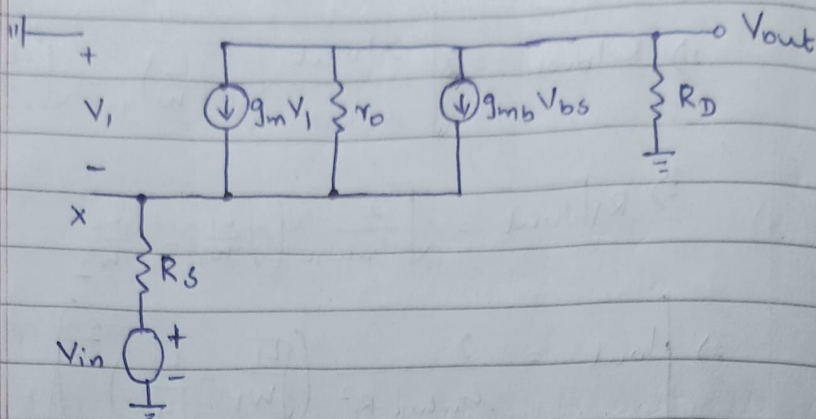

KVL at ip:

$$V_1 - \frac{V_{out}}{R_D} R_S + V_{in} = 0 \quad \text{--- (1)}$$

KVL at op:

$$r_o \left(-\frac{V_{out}}{R_D} - g_m V_1 - g_{mb} V_1 \right) - \frac{V_{out}}{R_D} R_S + V_{in} = V_{out} \quad \text{--- (2)}$$

from (1)

$$V_1 = V_{out} \cdot \frac{R_S}{R_D} - V_{in}$$

Substituting value of V_1 in (2).

$$r_o \left(-\frac{V_{out}}{R_D} - (g_m + g_{mb}) \left(V_{out} \cdot \frac{R_S}{R_D} - V_{in} \right) \right) - V_{out} \frac{R_S}{R_D} + V_{in} = V_{out}$$


$$\begin{aligned} \Rightarrow -V_{out} \cdot \frac{r_o}{R_D} - r_o (g_m + g_{mb}) \cdot \frac{R_S}{R_D} V_{out} - V_{out} \frac{R_S}{R_D} + V_{out} \\ = -V_{in} - (g_m + g_{mb}) r_o V_{in} \end{aligned}$$

$$2) V_{out} \left(\frac{r_o + (g_m + g_{mb})r_o R_S + R_S + R_D}{R_D} \right) = V_{in} (1 + r_o(g_m + g_{mb}))$$

$$2) \frac{V_{out}}{V_{in}} = \frac{[(g_m + g_{mb})r_o + 1] R_D}{r_o + (g_m + g_{mb})r_o R_S + R_S + R_D}$$

4. Explain the working of folded cascode circuit using large-signal analysis.

If V_{in} becomes more +ve
 $|I_{D1}|$ decreases, forcing
 I_{D2} to increase, hence
 decreasing V_{out} to drop.

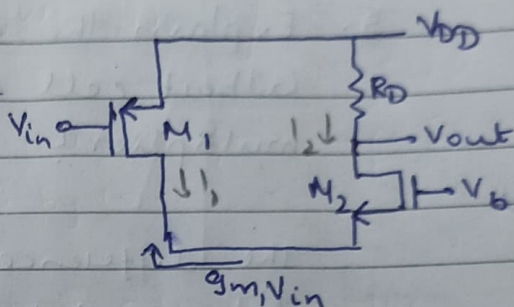

If V_{in} decreases from V_{DD} to zero, for $V_{in} > V_{DD} - |V_{th1}|$, M_1 is in SD and M_2 carries all of I_1 , yielding $V_{out} = V_{DD} - I_1 R_D$. For $V_{in} < V_{DD} - |V_{th1}|$, M_1 turns on in saturation,

$$I_{D2} = I_1 - \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_1 (V_{DD} - V_{in} - |V_{th1}|)^2$$


As V_{in} drops, I_{D2} decreases further, falling to zero, if $I_{D1} = I_1$.

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_1 (V_{DD} - V_{in1} - |V_{th1}|)^2 = I_1$$

Thus,


$$V_{in1} = V_{DD} - \sqrt{\frac{2I_1}{\mu_p C_{ox} (W/L)_1}} - |V_{th1}|$$

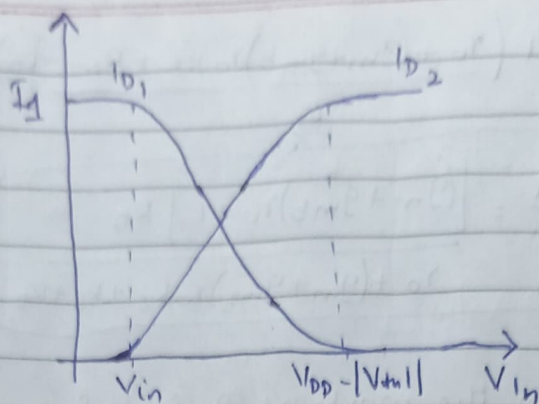If V_{in} falls below this level, I_{D1} tends to be greater than I_1 and M_1 enters the triode region.



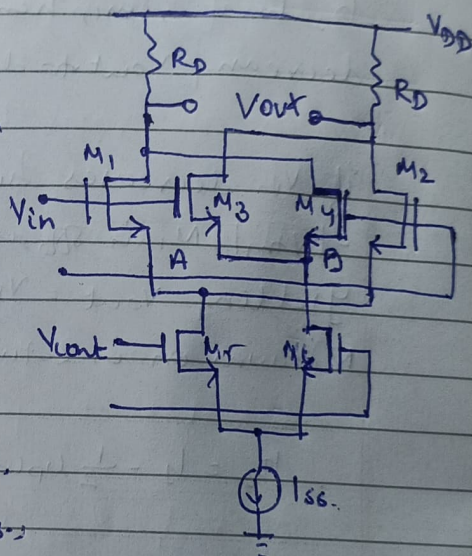5. Explain the operation of Gilbert cell. Can Gilbert cell operation as an analog voltage multiplier?

The difference between 2 terminals of V_{cont} steers a lot part of I_{SS} from V_{in} to V_{out} .



Since,

$$V_{out1} = R_D I_{D1} - R_D I_{D2}$$

$$V_{out2} = R_D I_{D4} - R_D I_{D3}$$

$$V_{out} = R_D (I_{D1} + I_{D4}) - R_D (I_{D2} + I_{D3})$$

where,

$$\frac{V_{out1}}{V_{in}} = -g_m R_D, \quad \frac{V_{out2}}{V_{in}} = +g_m R_D$$

Analog Voltage multiplier:

Since the gain of the circuit is a function of $V_{cont} = V_{cont1} - V_{cont2}$, we have

$V_{out} = V_{in} \cdot f(V_{cont})$. Expanding $f(V_{cont})$ in a Taylor series and retaining only the first-order term, αV_{cont} , we have $V_{out} = \alpha V_{in} V_{cont}$. Thus, the circuit can multiply voltages. This property accompanies any voltage-controlled variable-gain amplifier.

6. Assuming all the circuit to be symmetric, Plot V_{out} as V_{in1} and V_{in2} vary differentially from 0 to V_{DD}

