

## Experiment: Common Gate Amplifier

### **Aim:**

To implement a common gate amplifier of gain 10 and analyze its transient and ac characteristics.

### **Tool Used:**

LTspice

### **Theory:**

The common-gate (CG) amplifier for MOSFET is the analogue of the common base amplifier for BJT. Its popularity arises from its lower noise and ease of impedance matching.

For a Level 3 NMOS let's assume

$$V_{GS} = 0.6V$$

$$V_T = 0.4V$$

$$V_{DD} = 1.8V$$

$$K_n = 120\mu A/V^2,$$


Which gives a value of  $(W/L) = 416$  for  $1mA I_D$ .

Also, for these values  $g_m$  is attained as  $10m\Omega^{-1}$ , therefore for gain 10,  $R_D$  is taken as  $1K\Omega$ .

The value of  $V_{DS}$  should be maintained above  $(V_{GS} - V_T = 0.6 - 0.4 = 0.2V)$  for the transistor to stay in saturation region.

As  $W/L$  is 416, the width is taken as  $416\mu m$  and the length is taken as  $1\mu m$ .

## Circuit Schematic:

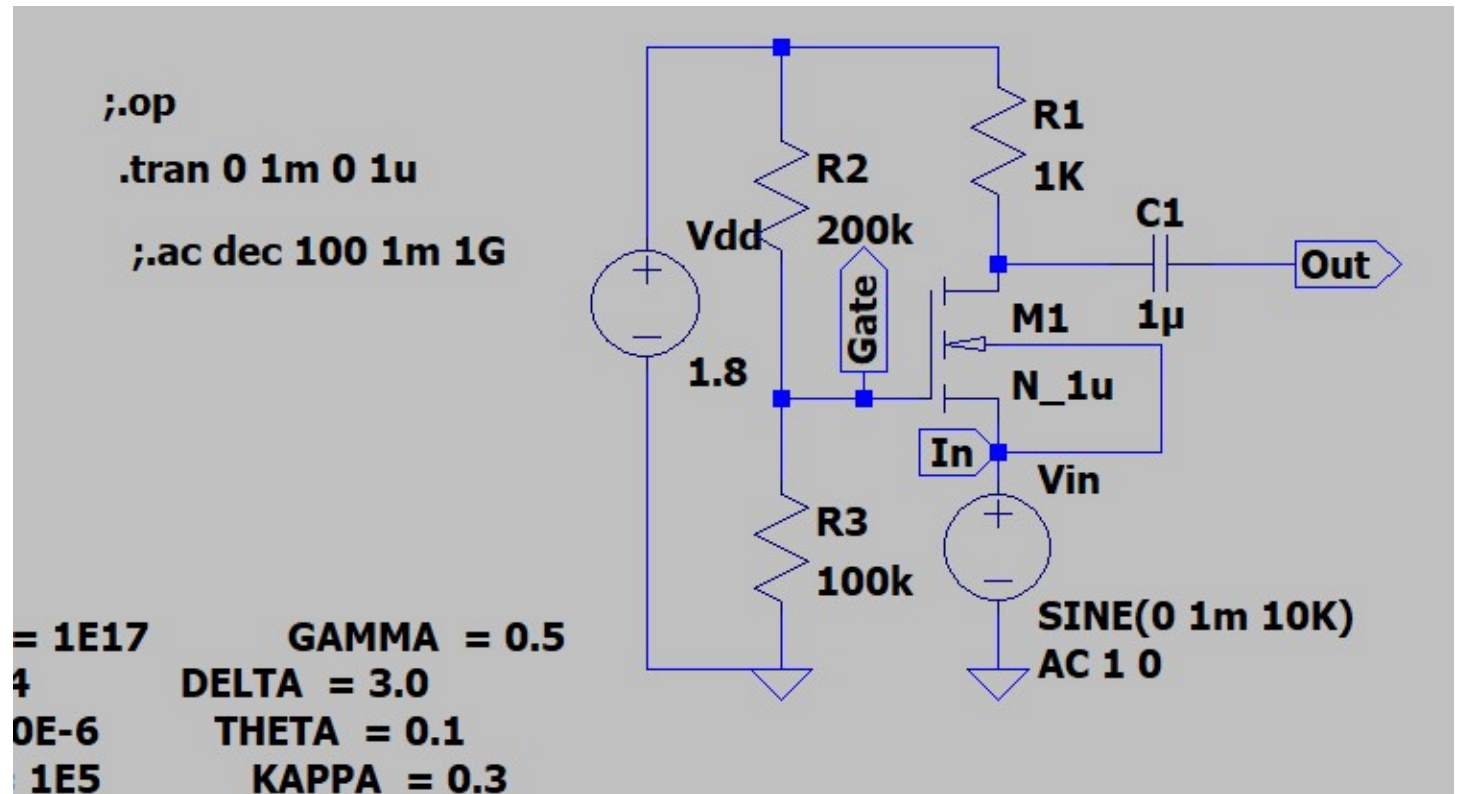


## Output Waveforms:


DC operating Point

--- Operating Point ---		
V(n002):	0.351845	voltage
V(gate):	0.6	voltage
V(in):	0	voltage
V(n001):	1.8	voltage
V(out):	3.51845e-007	voltage
Id(M1):	0.00144818	device_current
Ig(M1):	0	device_current
Ib(M1):	-3.61845e-013	device_current
Is(M1):	-0.00144818	device_current
I(C1):	-3.51845e-019	device_current
I(R3):	6e-006	device_current
I(R2):	6e-006	device_current
I(R1):	0.00144815	device_current
I(Vdd):	-0.00145415	device_current
I(Vin):	0.00144815	device_current

## Transient characteristics

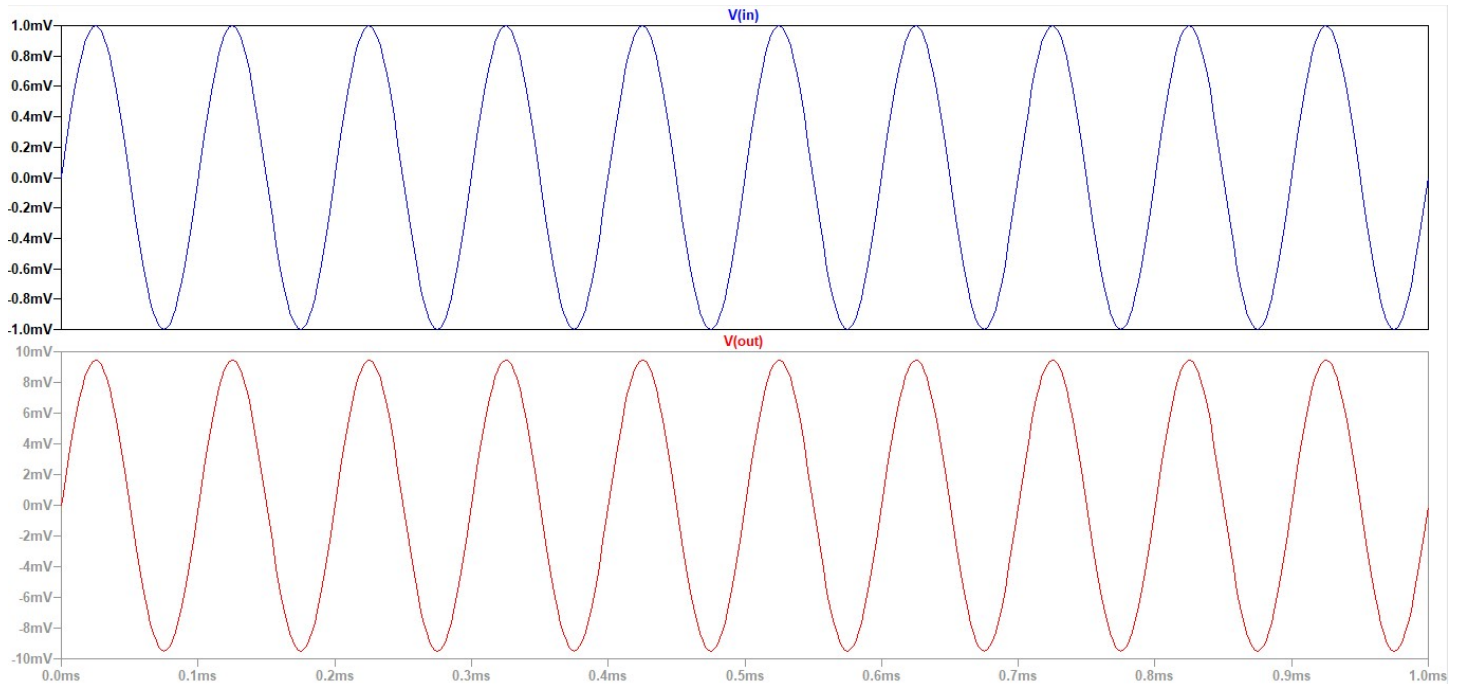

## AC Analysis

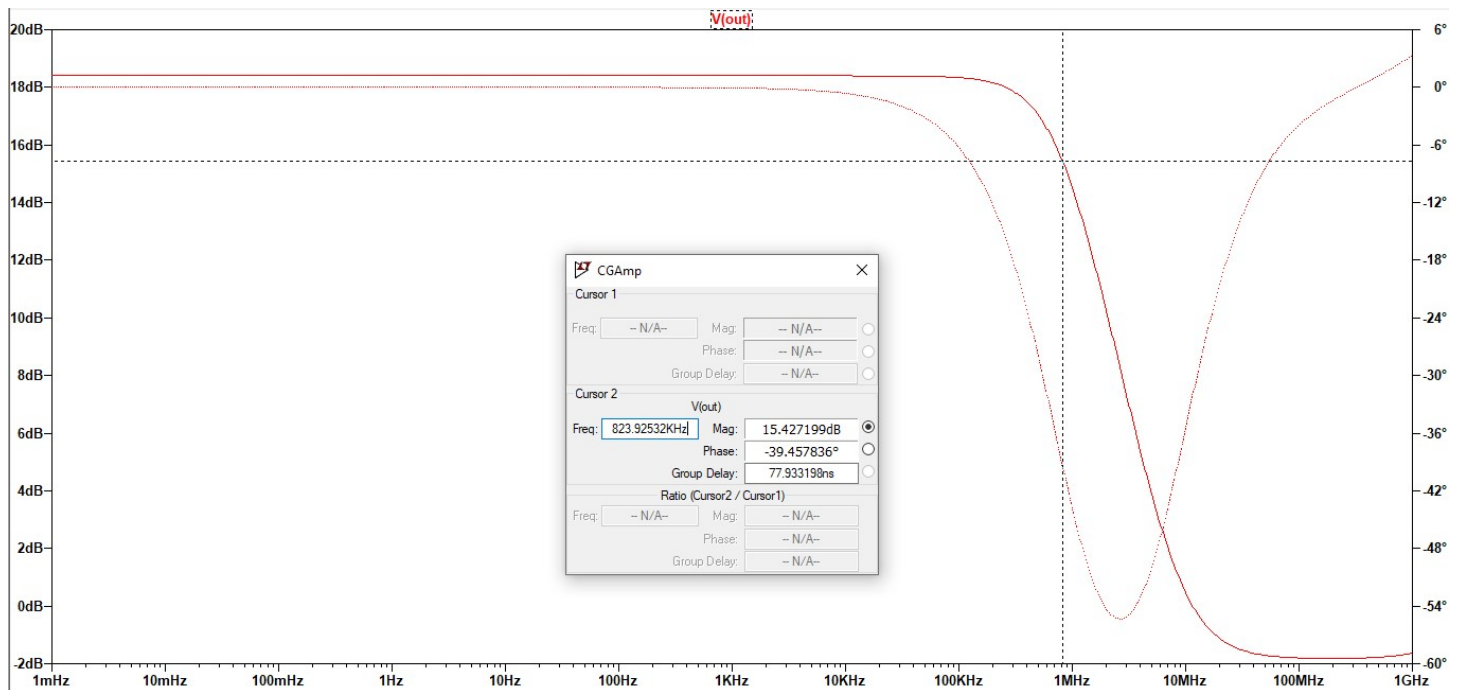

## Result:

The circuit is designed for a gain of 10 and the output is verified to be correct. The transient and AC characteristics are visualized.

Bandwidth,  $F_c = 823\text{KHz}$ .