

# Experiment: CMOS and Resistive load Inverter Characteristics

## PART-A

### **Aim:**

To implement a CMOS inverter of level (1, 3 and 54) and analyze its transient and dc characteristics.


### **Tool Used:**

LTspice

### **Theory:**


In CMOS technology, both N-type and P-type transistors are used to design logic functions. The same signal which turns ON a transistor of one type is used to turn OFF a transistor of the other type. This characteristic allows the design of logic devices using only simple switches, without the need for a pull-up resistor. In CMOS inverter an n-type MOSFET acts as a pull-down transistor between the output and the low voltage power supply rail ( $V_{ss}$  or quite often ground). Instead of the load resistor of Resistive Inverter, CMOS inverter has a p-type MOSFET in a pull-up transistor between the output and the higher-voltage rail (often named  $V_{dd}$ ).

### **Circuit Schematic: [ Level 1 ]**

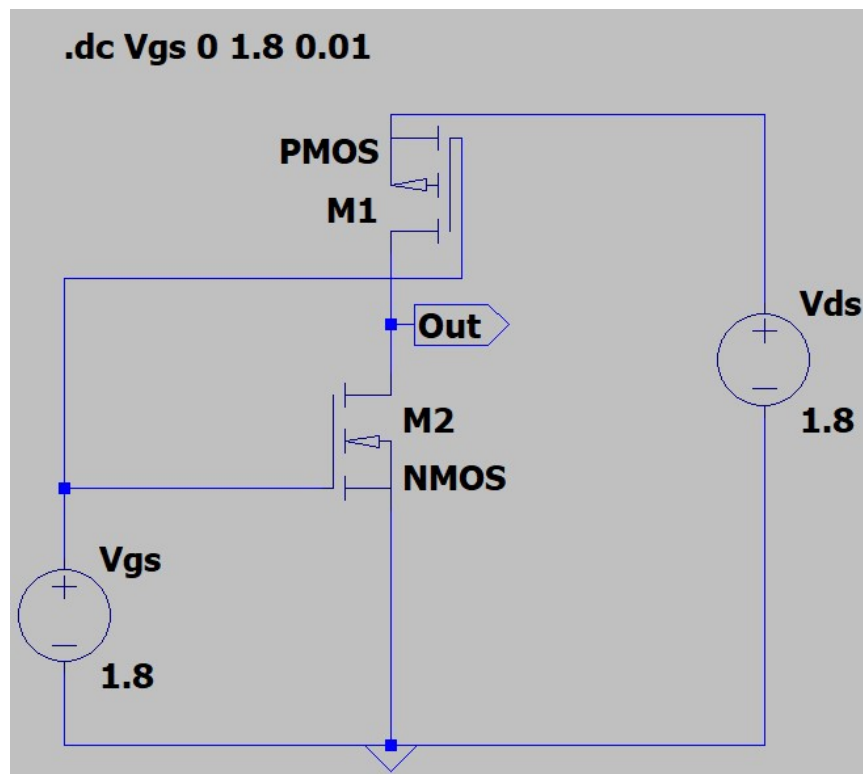

 
## Output Waveforms:


Dc Transfer characteristics ( $V_{gs}$  vs.  $V_{out}$ )



Transient characteristics

 


## Circuit Schematic: [ Level 3]

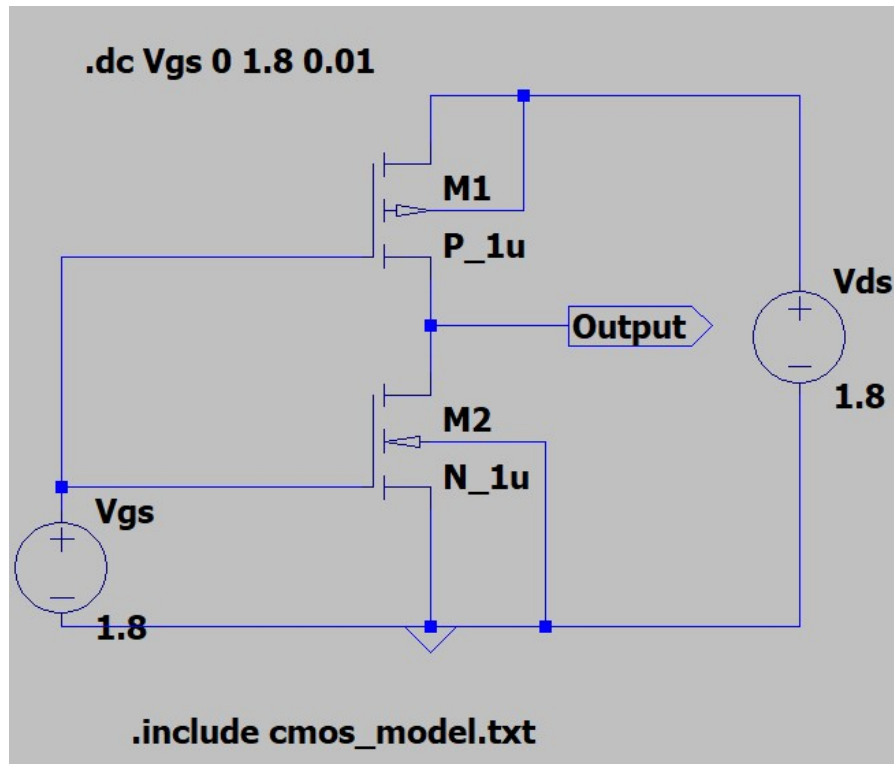

 
## Output Waveforms:


Dc Transfer characteristics ( $V_{gs}$  vs.  $V_{out}$ ) for  $(W/L)_p / (W/L)_n = 5$



## Transient characteristics

 


## Circuit Schematic: [ Level 54]

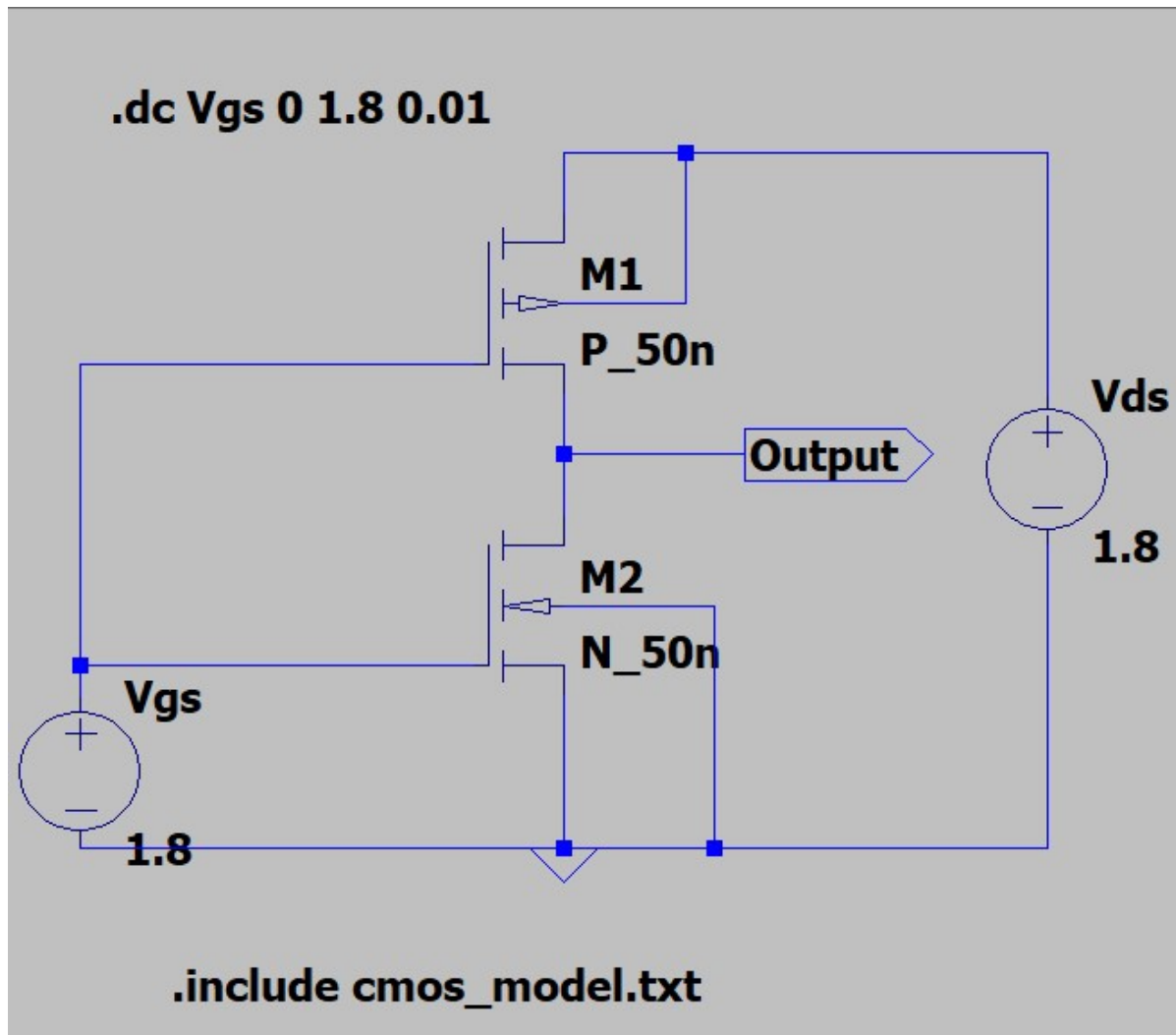

 
## Output Waveforms:

Dc Transfer characteristics ( $V_{gs}$  vs.  $V_{out}$ ) for  $(W/L)_p / (W/L)_n = 2.2$



## Transient characteristics

 

## Result:

The circuit is stimulated for 3 levels of CMOS inverter and the transient and dc characteristics are visualized.

## PART-B

### Aim:

To implement a Resistive Load inverter and analyze its transient and dc characteristics.


### Tool Used:

LTspice

### Theory:


The basic structure of a resistive load inverter is shown in the figure given below. Here, enhancement type nMOS acts as the driver transistor. The load consists of a simple linear resistor  $R_L$ . The power supply of the circuit is  $V_{DD}$  and the drain current  $I_D$  is equal to the load current  $I_R$ . When the input of the driver transistor is less than threshold voltage  $V_{TH}$  ( $V_{in} < V_{TH}$ ), driver transistor is in the cut – off region and does not conduct any current. So, the voltage drop across the load resistor is ZERO and output voltage is equal to the  $V_{DD}$ . Now, when the input voltage increases further, driver transistor will start conducting the non-zero current and nMOS goes in saturation region.

### Circuit Schematic:

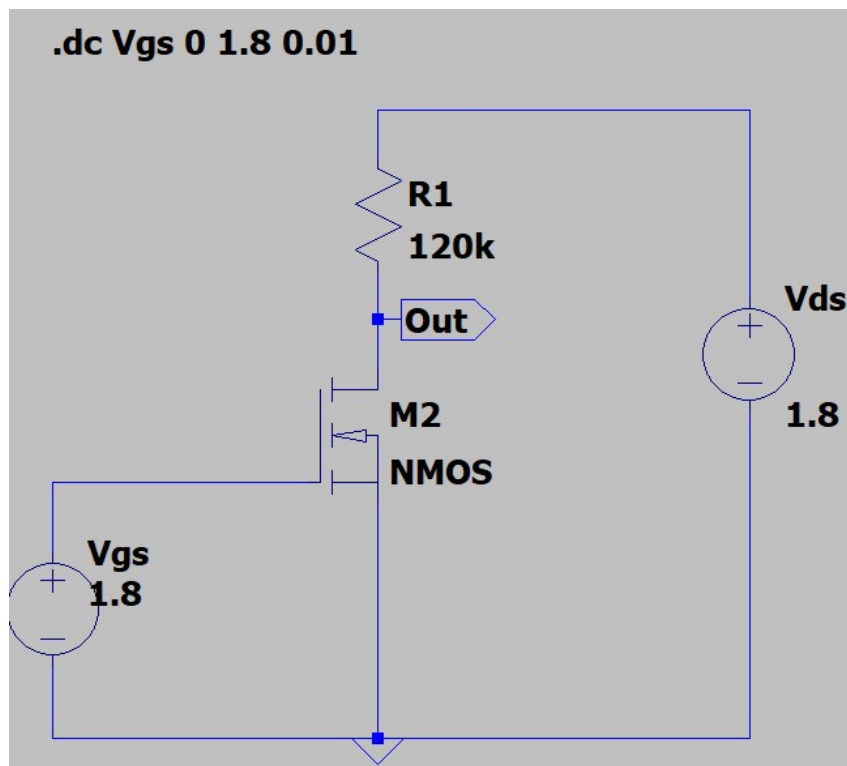

 
## Output Waveforms:

Dc Transfer characteristics ( $V_{gs}$  vs.  $V_{out}$ )



Transient characteristics

 

## Result:

The circuit is stimulated with 120k resistor and the transient and dc characteristics are visualized.