

Experiment: Differential Amplifier

Aim:

To implement a differential amplifier of gain 10 and analyze its transient characteristics.

Tool Used:

LTspice

Theory:

Differential amplifiers apply gain not to one input signal but to the difference between two input signals. This means that a differential amplifier naturally eliminates noise or interference that is present in both input signals.

For a Level 3 NMOS, PMOS let's assume

$$V_T = 0.4V$$

$$V_{DD} = 1.8V$$

$$K_n = 120\mu A/V^2,$$

$$K_p = 120\mu A/V^2,$$

Which implies

$$r_{01} = 1/\lambda_n I_D$$


$$r_{02} = 1/\lambda_p I_D$$

Which gives the value of R_{out} to be 16.66Kohm

Which gives a value of $(W/L) = 30$ for 100uA I_D .

Hence with this value of W/L we get a V_{GS} of 0.635V

Circuit Schematic:

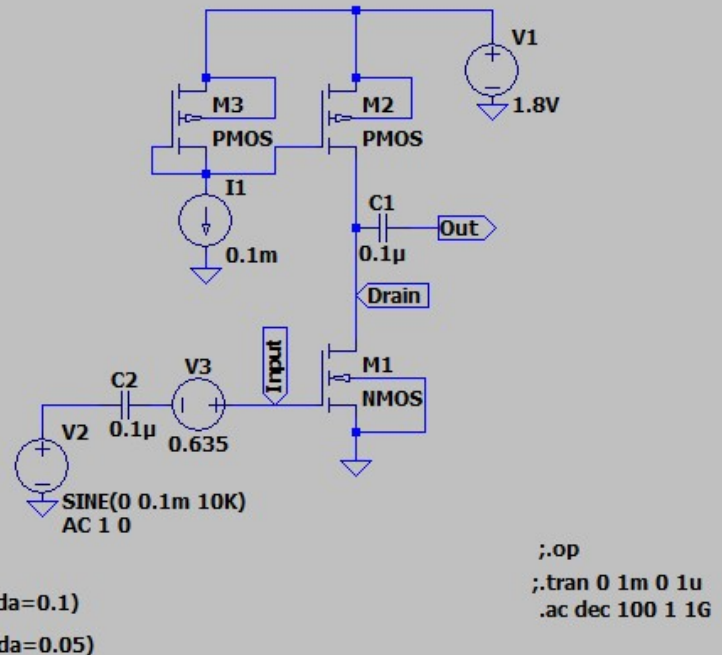


Output Waveforms:

--- Operating Point ---

V(n001):	1.8	voltage
V(n002):	0.15892	voltage
V(drain):	0.218448	voltage
V(out):	2.18448e-008	voltage
V(input):	0.635	voltage
V(n003):	0	voltage
V(n004):	0	voltage
Id(M1):	9.97249e-005	device_current
Ig(M1):	0	device_current
Ib(M1):	-2.28446e-013	device_current
Is(M1):	-9.97249e-005	device_current
Id(M3):	0.0001	device_current
Ig(M3):	-0	device_current
Ib(M3):	1.65108e-012	device_current
Is(M3):	-0.0001	device_current
Id(M2):	9.97249e-005	device_current
Ig(M2):	-0	device_current
Ib(M2):	1.59155e-012	device_current
Is(M2):	-9.97249e-005	device_current
I(C2):	0	device_current
I(C1):	-2.18448e-020	device_current
I(I1):	0.0001	device_current
I(V3):	0	device_current
I(V2):	0	device_current
I(V1):	-0.000199725	device_current

Transient characteristics

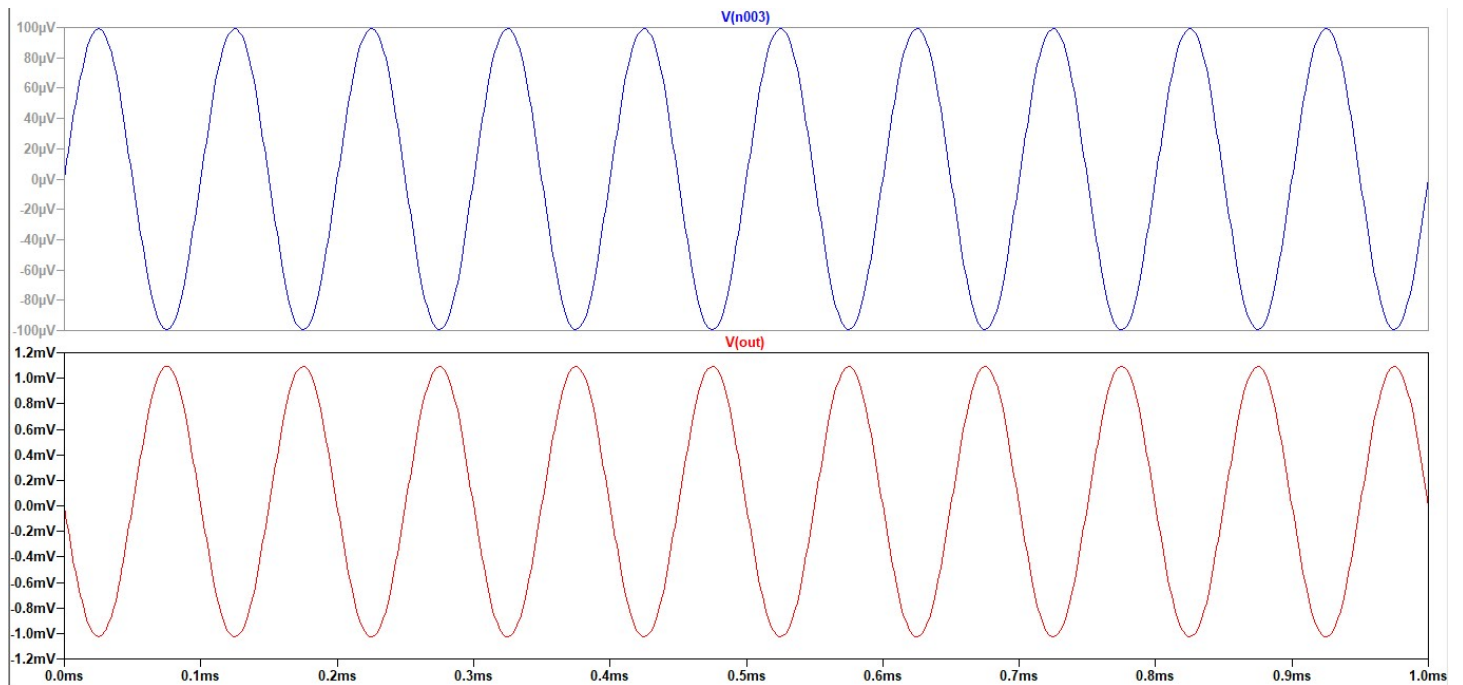

Result:

The circuit is designed for a gain of 10 and the output is verified to be correct.