

# INVERTING AND NON-INVERTING AMPLIFIER USING OP-AMP

## AIM:

- 1) Design an Inverting and Non Inverting Amplifier using Op Amp using F/B network.
- 2) Determine the Bandwidth of Amplifier using AC analysis.
- 3) Evaluate the open loop gain, loop gain and close loop gain of both the amplifier ( $V_{FB}/V_{TEST}$ ) and do AC analysis.
- 4) Comment on the stability of the Feedback Amplifier.

## APPARATUS REQUIRED:

LTSpice Software.

## THEORY:

An inverting amplifier (also known as an inverting operational amplifier or an inverting op-amp) is a type of operational amplifier circuit which produces an output which is out of phase with respect to its input by  $180^\circ$ . The voltage gain of the inverting amplifier is,

$$A_v = \frac{-R_f}{R_1}$$


Feedback control of the non-inverting operational amplifier is achieved by applying a small part of the output voltage signal back to the inverting (–) input terminal via a  $R_f - R_2$  voltage divider network, again producing negative feedback. This closed-loop configuration produces a non-inverting amplifier circuit with very good stability, a very high input impedance,  $R_{in}$  approaching infinity, as no current flows into the positive input terminal, (ideal conditions) and a low output impedance. The voltage gain of the non inverting amplifier is,

$$A_v = 1 + \frac{R_f}{R_1}$$


INVERTING AMPLIFIER:

OPEN LOOP


CIRCUIT:

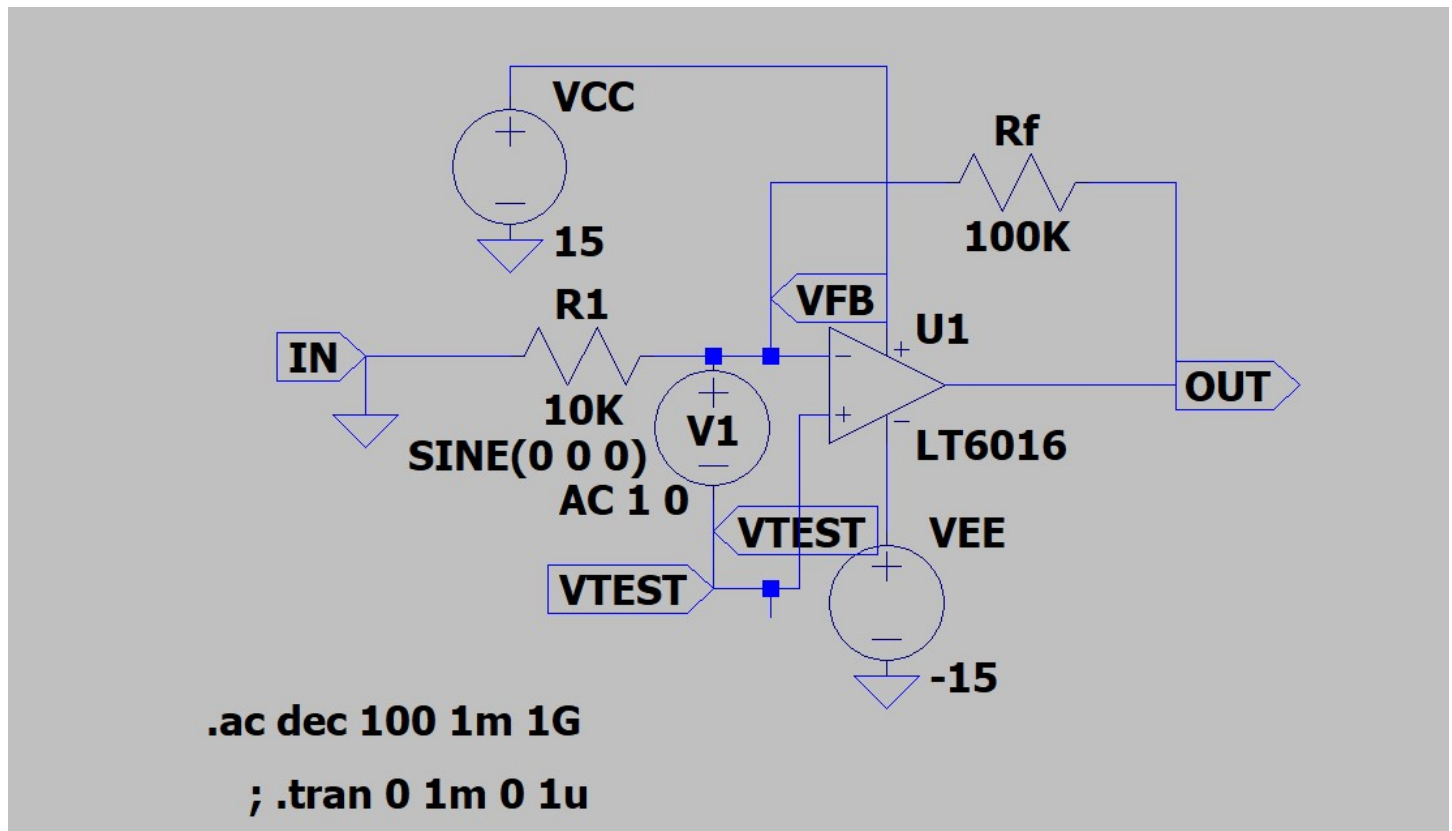

OUTPUT:

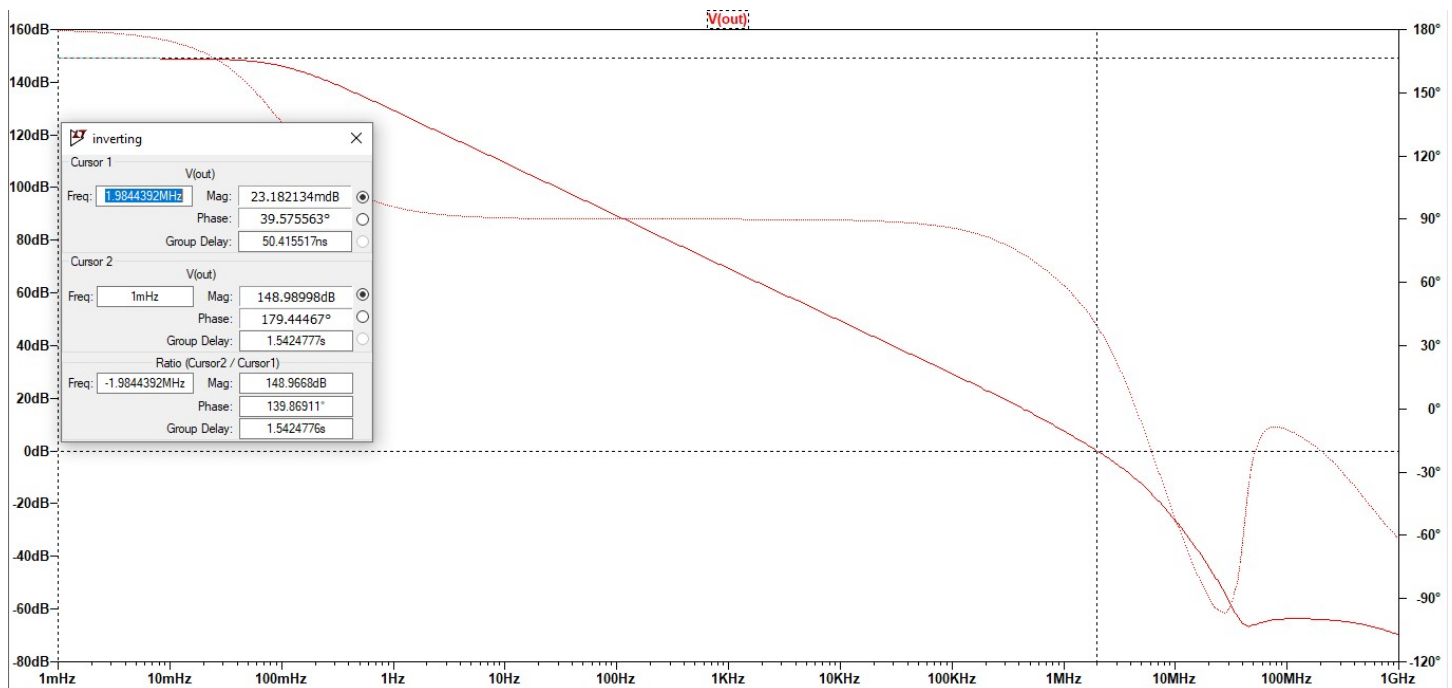


$$V_{fb} / V_{Test}$$

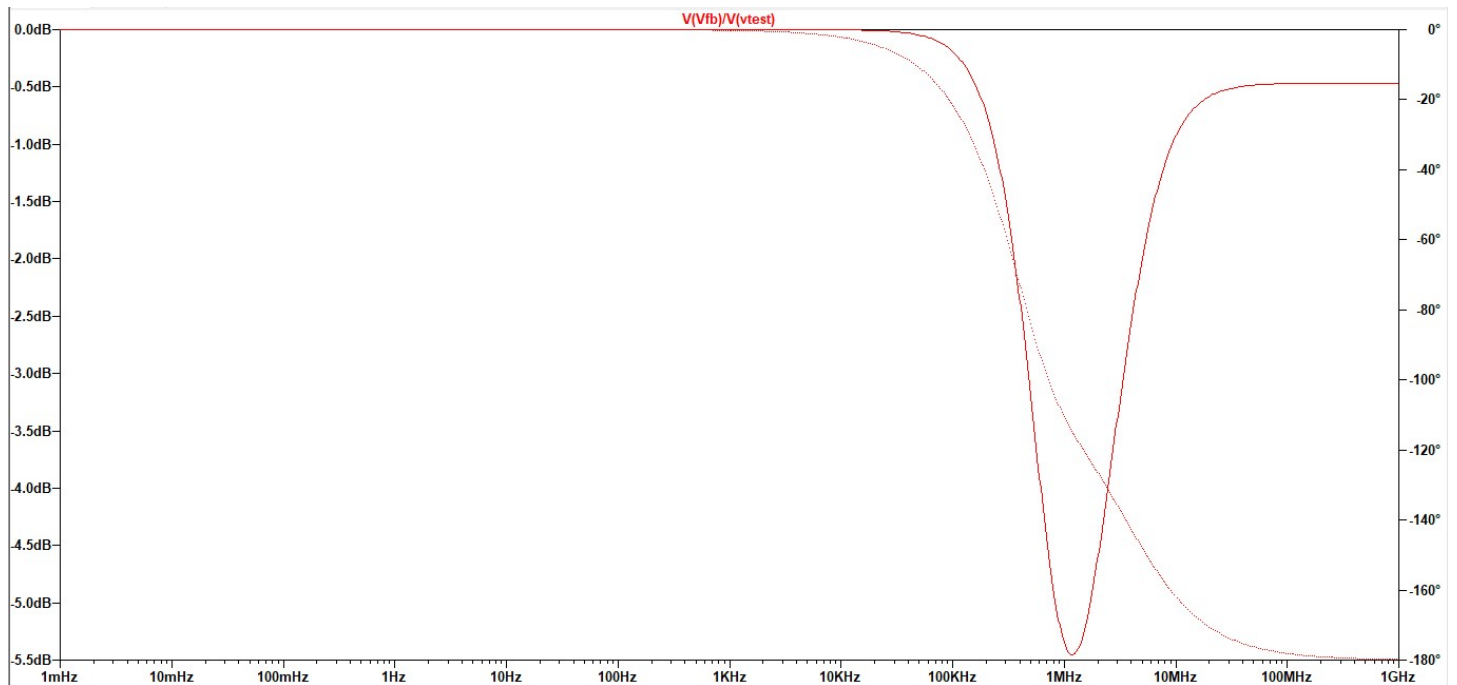


CLOSED LOOP:


CIRCUIT:

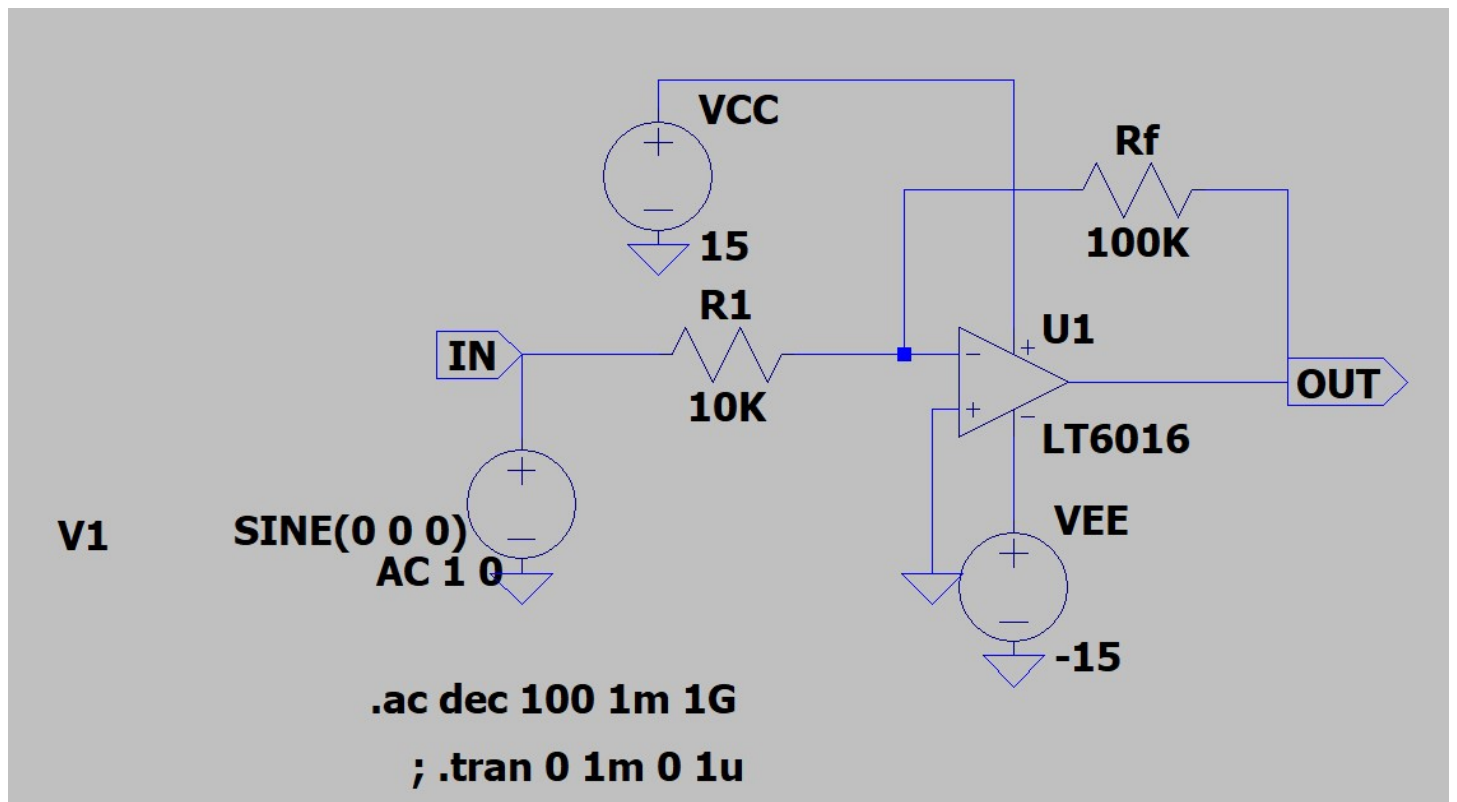

## OUTPUT:

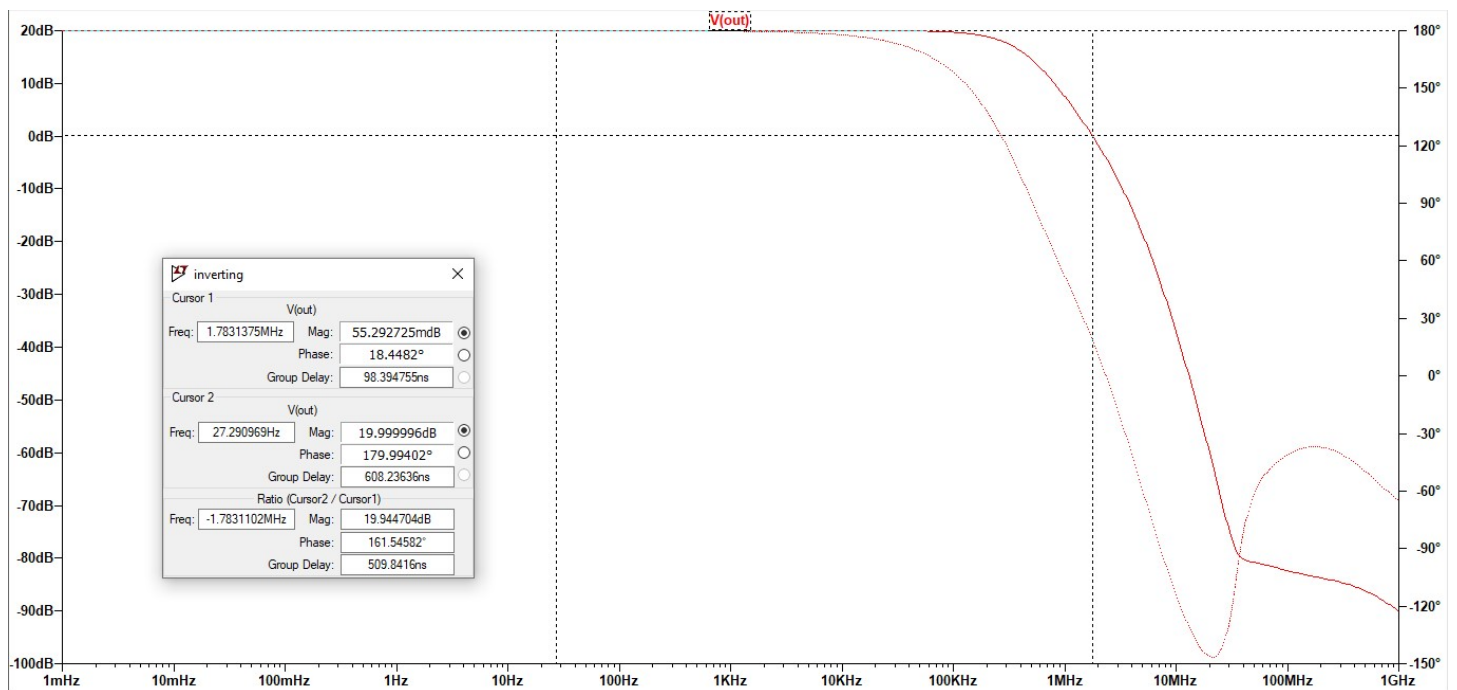

## TRANSIENT:

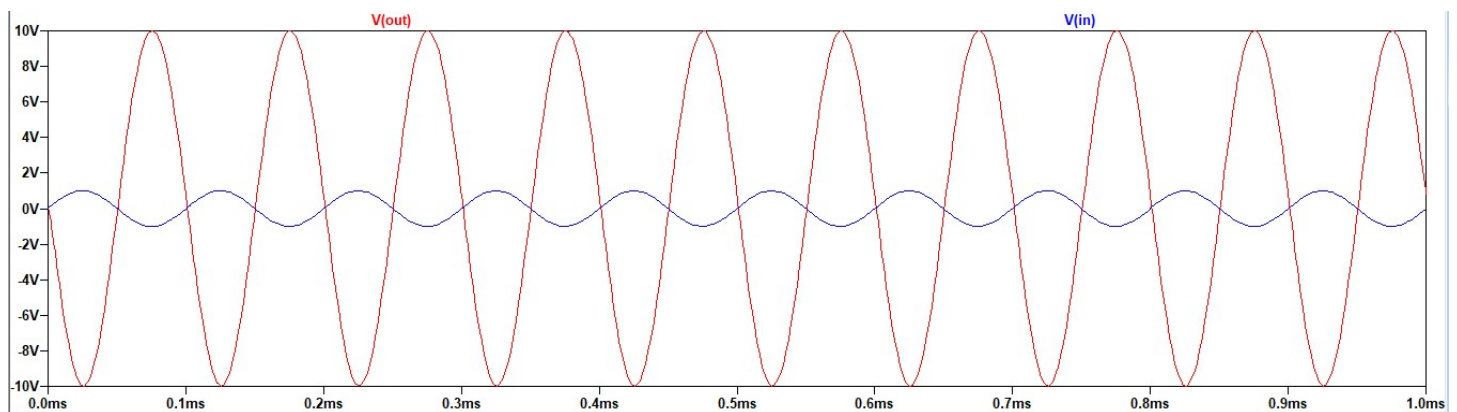

## Observation:

Open loop:  $W_{gc} = 1.984\text{MHz}$ . The phase doesn't cross -180 degrees so the system is stable.


Closed loop:  $W_{gc} = 1.784\text{MHz}$ . The phase doesn't cross -180 degrees so the system is stable.

Closed loop gain = 10


NON INVERTING AMPLIFIER:

OPEN LOOP


CIRCUIT:

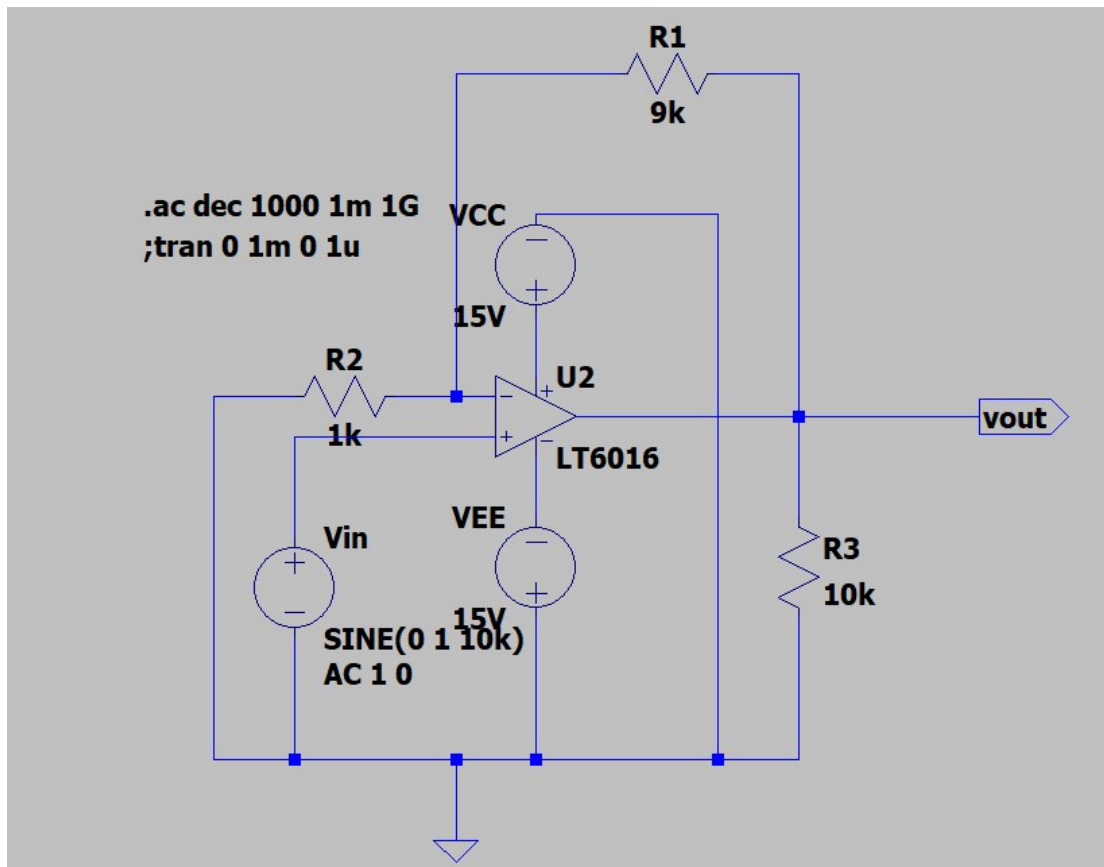

OUTPUT:

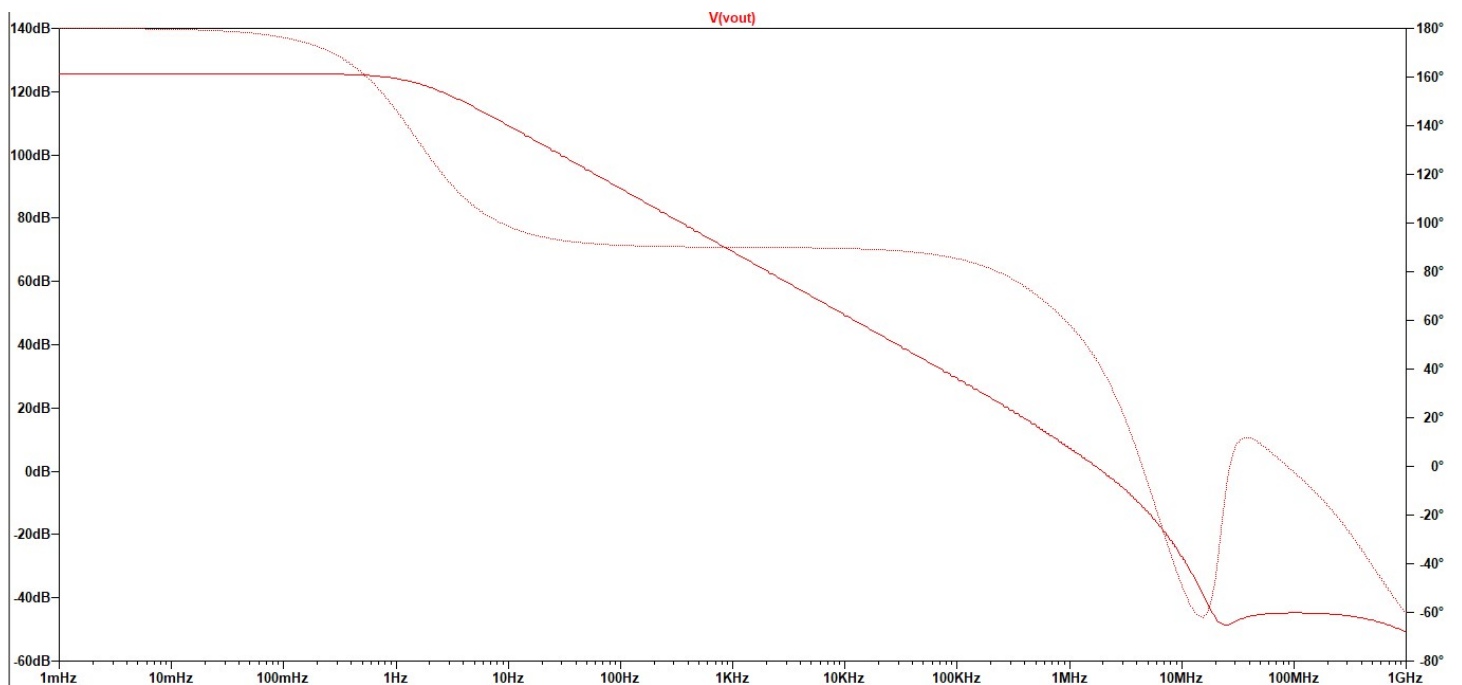


$V_{fb} / V_{Test}$

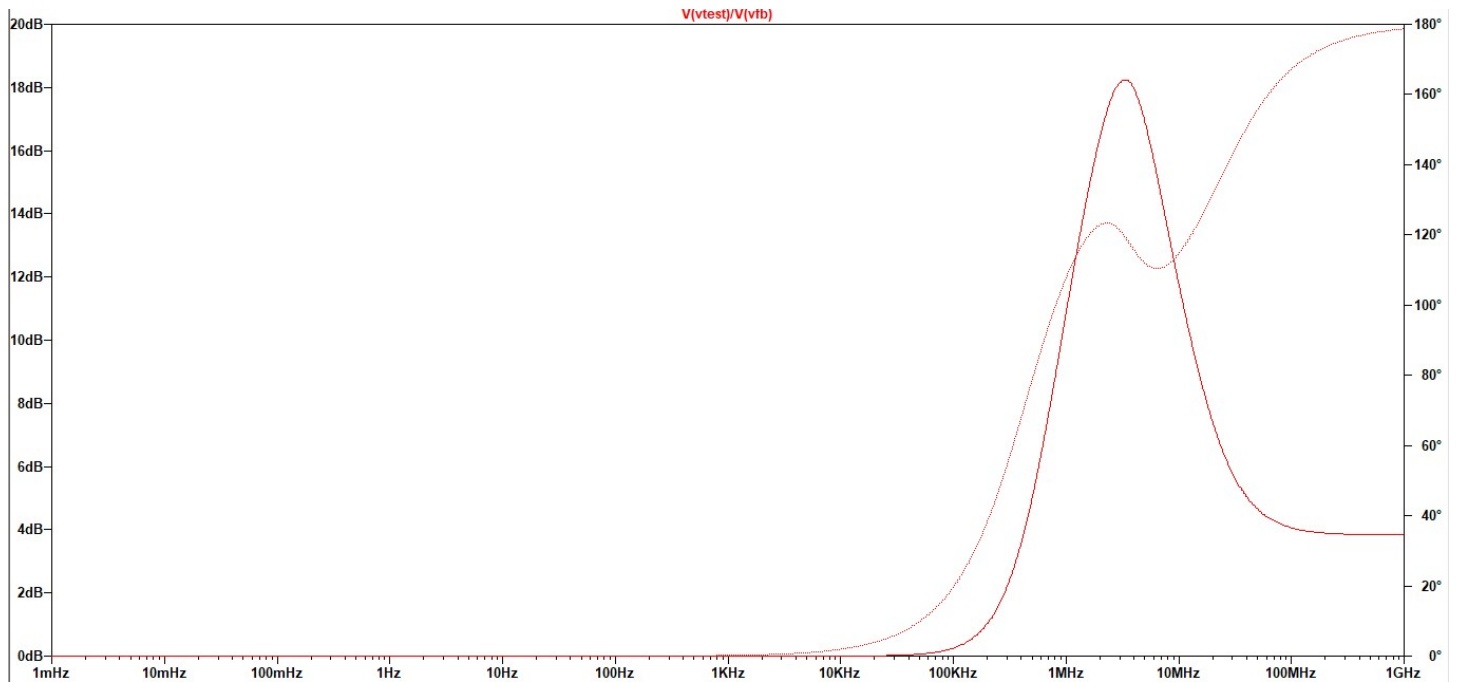


CLOSED LOOP:


CIRCUIT:

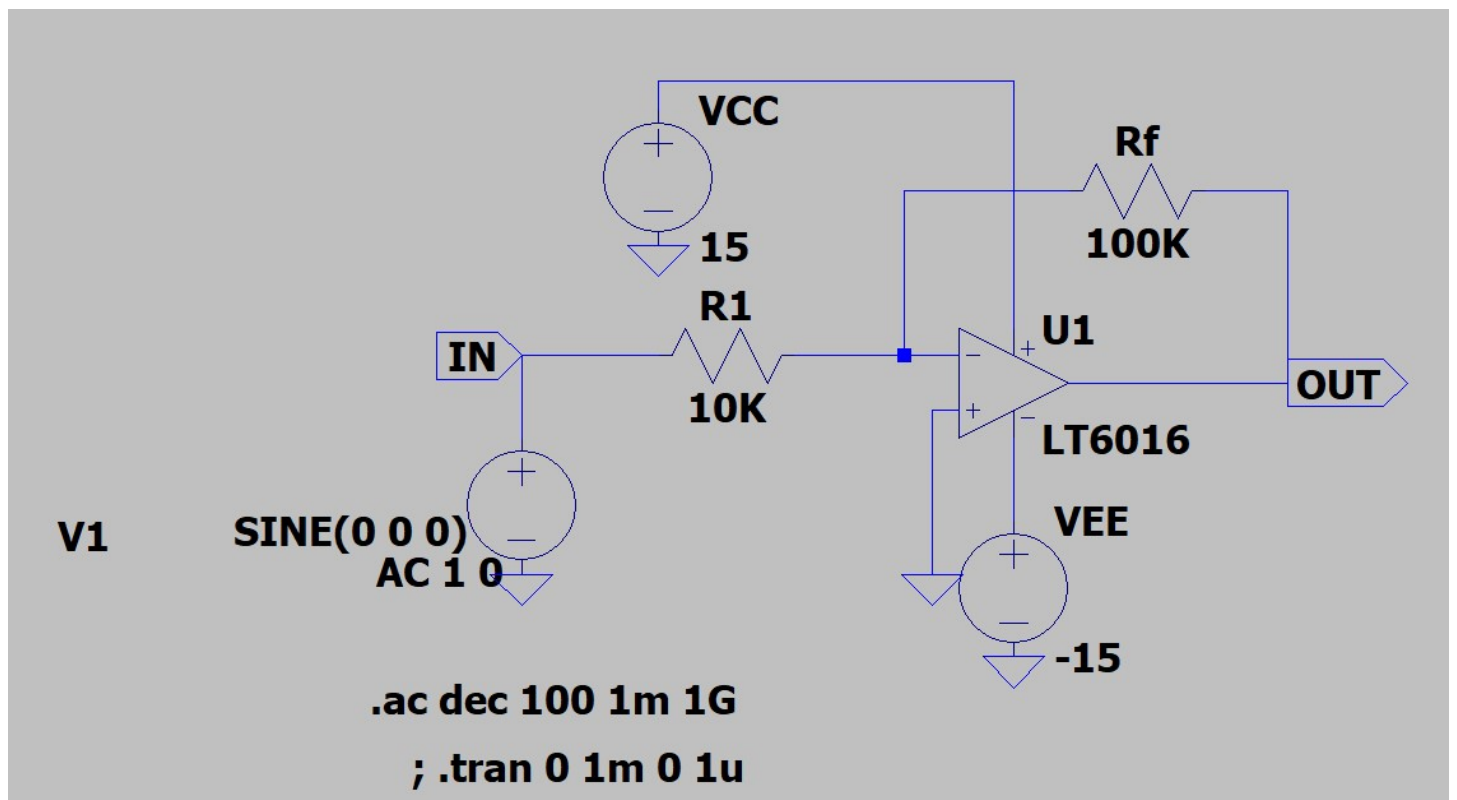

## OUTPUT:

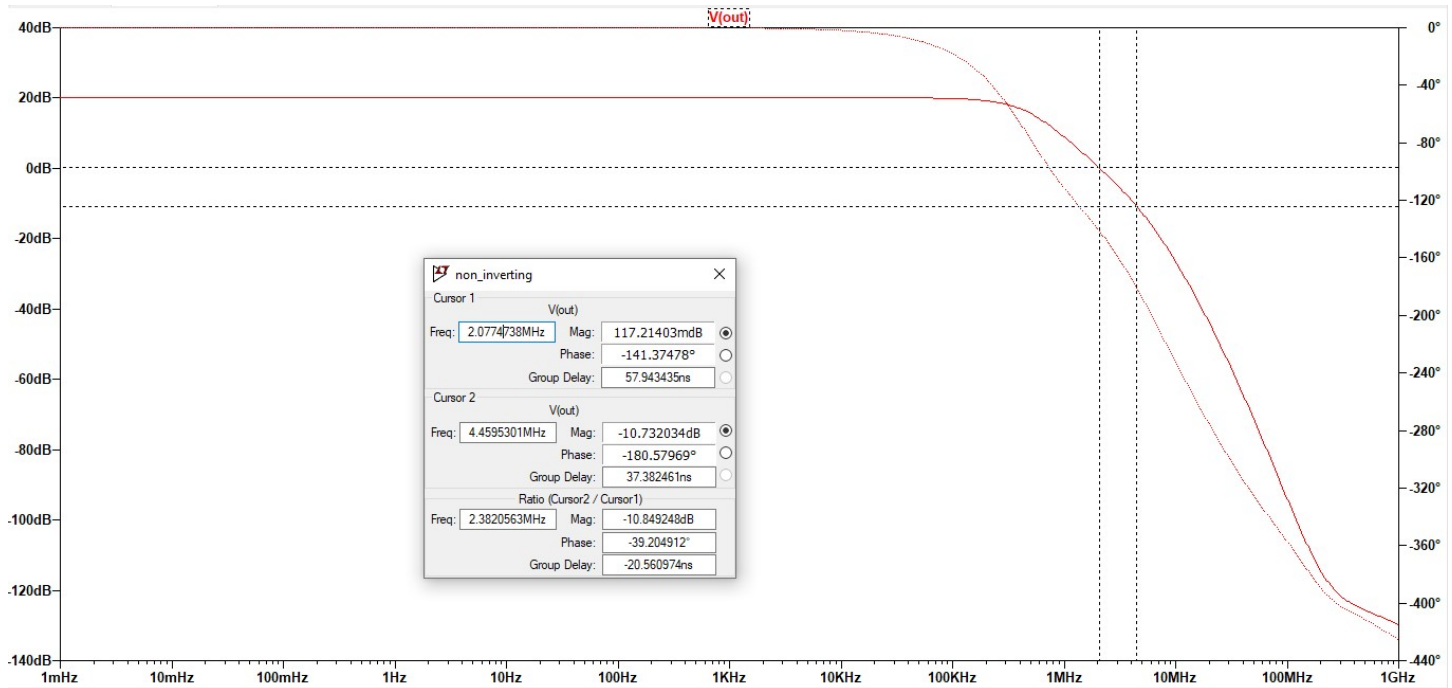

## TRANSIENT:

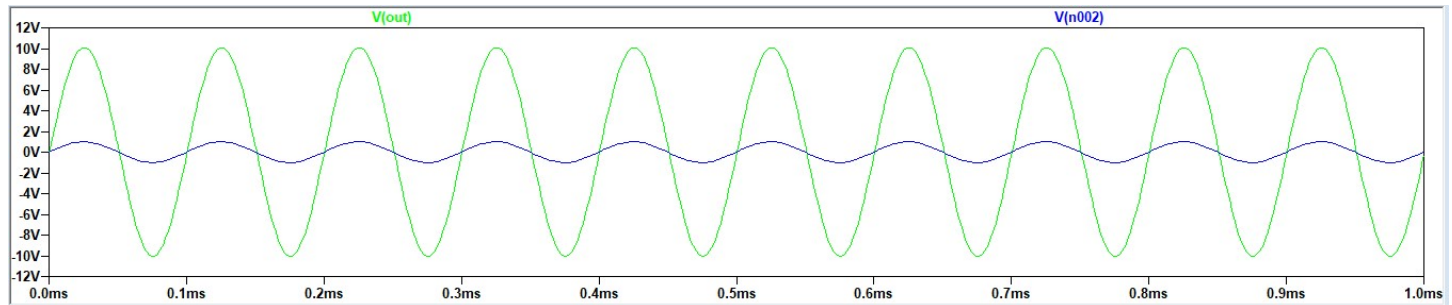

## Observation:

Open loop: Open loop:  $W_{gc} = 1.984\text{MHz}$ . The phase doesn't cross  $-180$  degrees so the system is stable.

Closed loop:  $W_{gc} = 2.07\text{ MHz}$ ,  $W_{pc} = 4.45\text{ MHz}$ .  $W_{gc} < W_{pc}$ , so the system is stable.

Phase Margin =  $-39.2$  degrees

Gain Margin =  $10\text{dB}$

Closed loop gain =  $10$

## Result:

The Experiment has been performed with both configuration of OpAmp and found to be correct.