

Experiment: 150nm pMOS and nMOS Characteristics

PART-A

Aim:

To implement a pMOS transistor and analyze its output and transfer characteristics.


Tool Used:

LTspice

Theory:


PMOS transistors operate by creating an inversion layer in an n-type transistor body. This inversion layer, called the p-channel, can conduct holes between p-type "source" and "drain" terminals. The p-channel is created by applying a negative voltage to the third terminal, called the gate. 150nm represent the minimum feature size of the NMOS transistor.

Circuit Schematic:

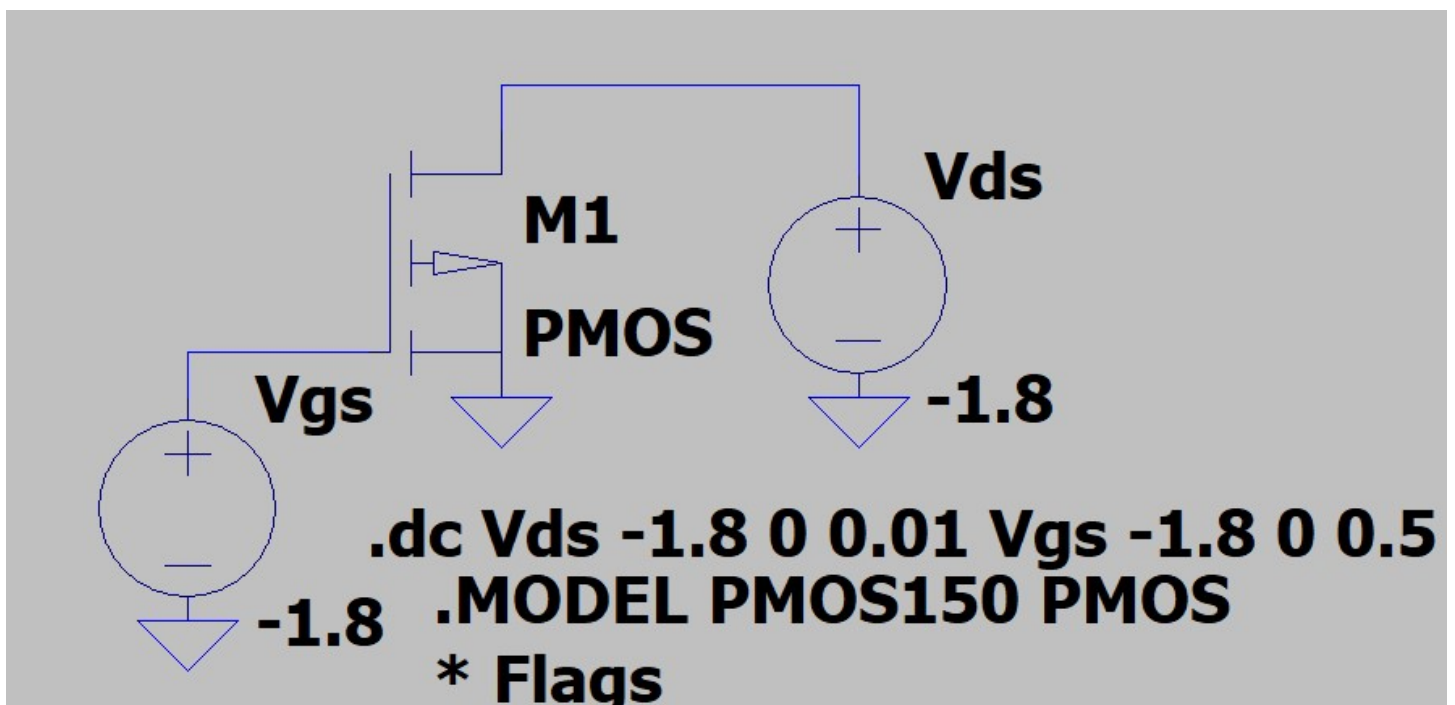


Output Waveforms:

Output characteristics (V_{ds} vs. I_d)

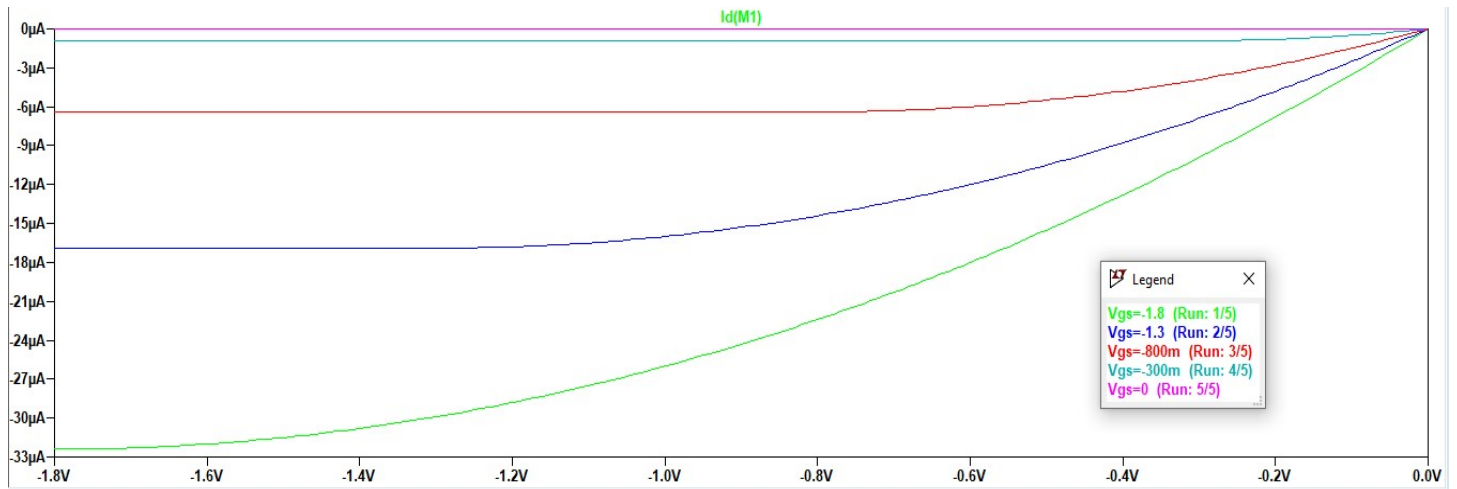

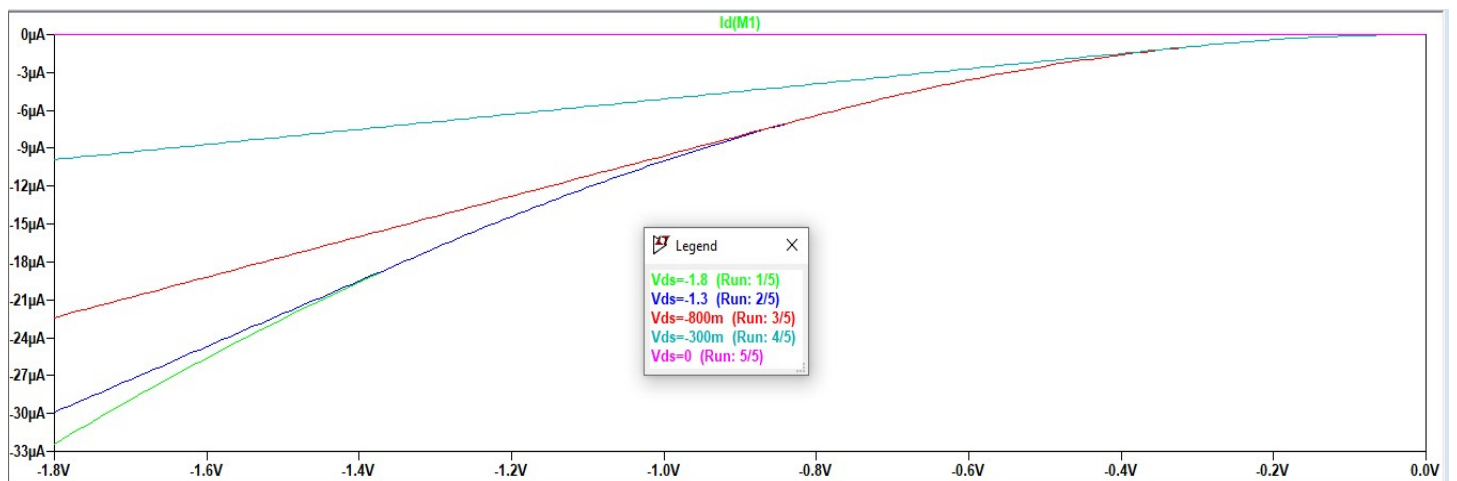Transfer characteristics (V_{gs} vs. I_d)



Result:

The circuit is stimulated using 150nm technology node and the output and transfer characteristics are visualized.

PART-B

Aim:

To implement an nMOS transistor and analyze its output and transfer characteristics.


Tool Used:

LTspice

Theory:


nMOS transistors operate by creating an inversion layer in a p-type transistor body. This inversion layer, called the n-channel, can conduct electrons between n-type "source" and "drain" terminals. The n-channel is created by applying voltage to the third terminal, called the gate. 150nm represent the minimum feature size of the NMOS transistor.

Circuit Schematic:

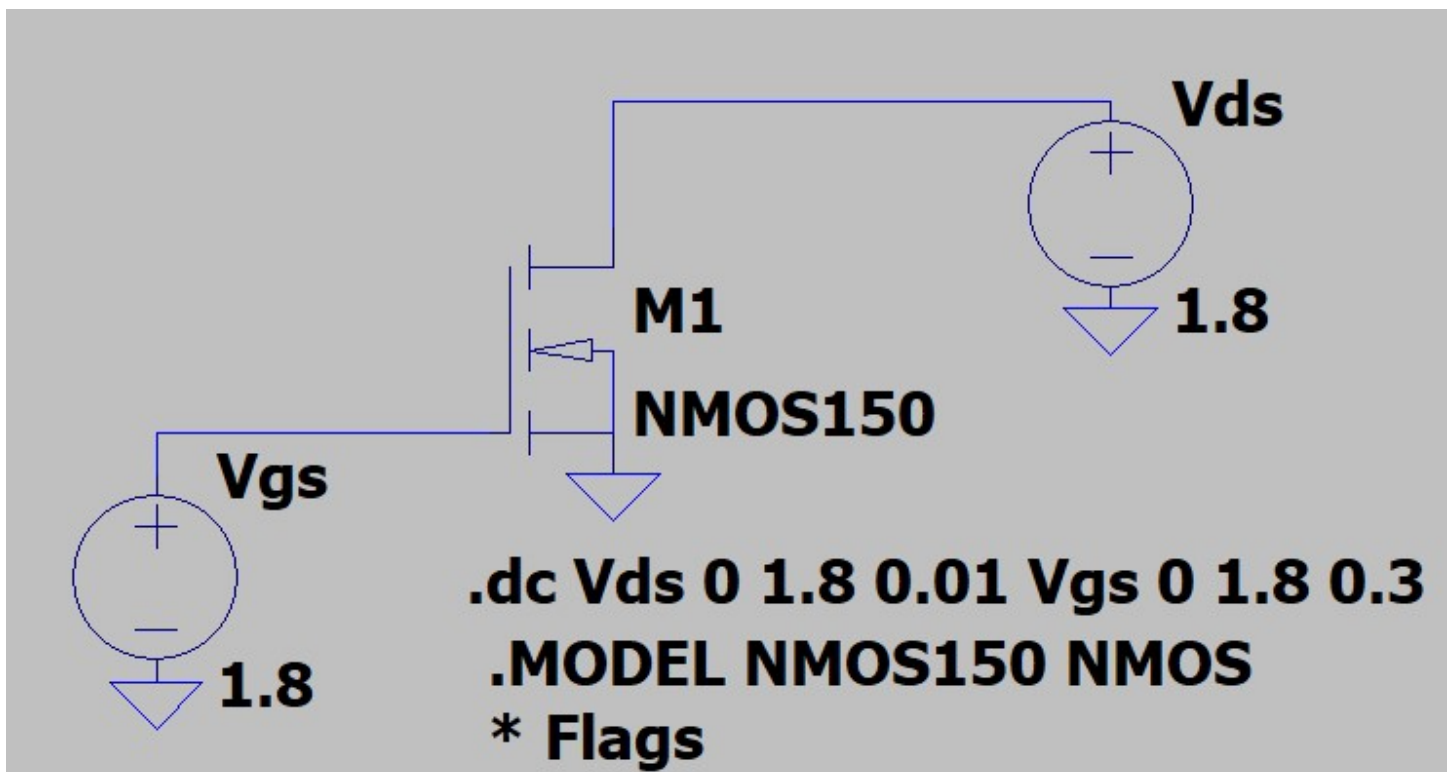


Output Waveforms:

Output characteristics (V_{ds} vs. I_d)

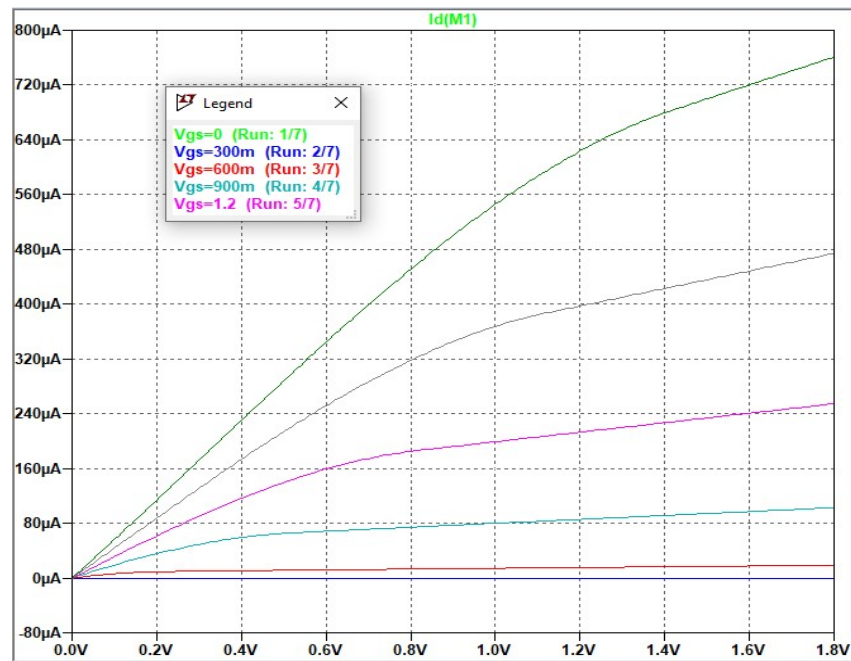

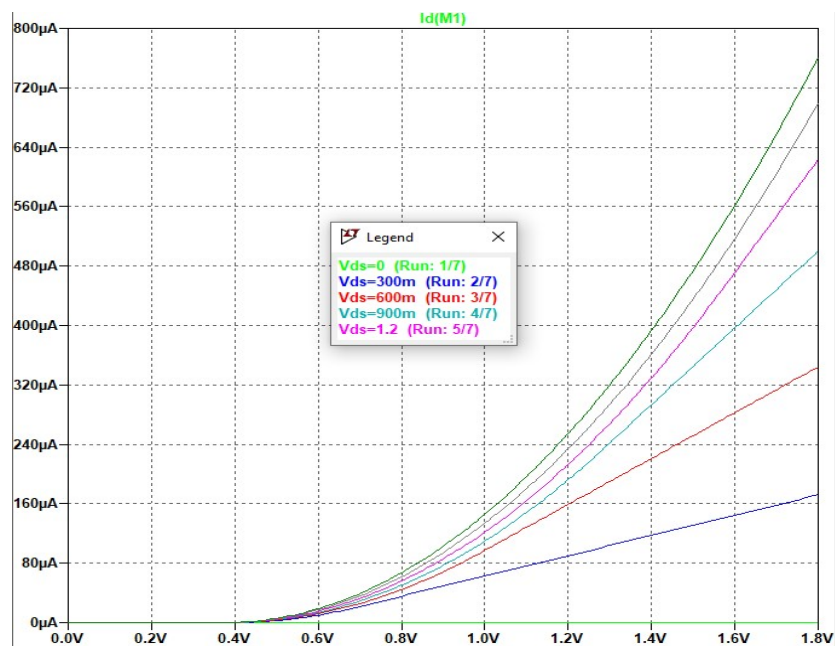Transfer characteristics (V_{gs} vs. I_d)



Result:

The circuit is stimulated using 150nm technology node and the output and transfer characteristics are visualized.