

Experiment: Common Source Amplifier

Aim:

To implement a common source amplifier of gain 10 and analyze its transient and ac characteristics.

Tool Used:

LTspice

Theory:

The common-source (CS) amplifier for MOSFET is the analogue of the common emitter amplifier for BJT. Its popularity arises from its high gain, and that by cascading a number of them, larger amplification of the signal can be achieved.

For a Level 3 NMOS let's assume

$$V_{GS} = 0.6V$$

$$V_T = 0.4V$$

$$V_{DD} = 1.8V$$

$$K_n = 120\mu A/V^2,$$


Which gives a value of $(W/L) = 416$ for $1mA I_D$.

Also, for these values g_m is attained as $10m\Omega^{-1}$, therefore for gain 10, R_D is taken as $1K\Omega$.

The value of V_{DS} should be maintained above $(V_{GS} - V_T = 0.6 - 0.4 = 0.2V)$ for the transistor to stay in saturation region.

As W/L is 416, the width is taken as $416\mu m$ and the length is taken as $1\mu m$.

Circuit Schematic:

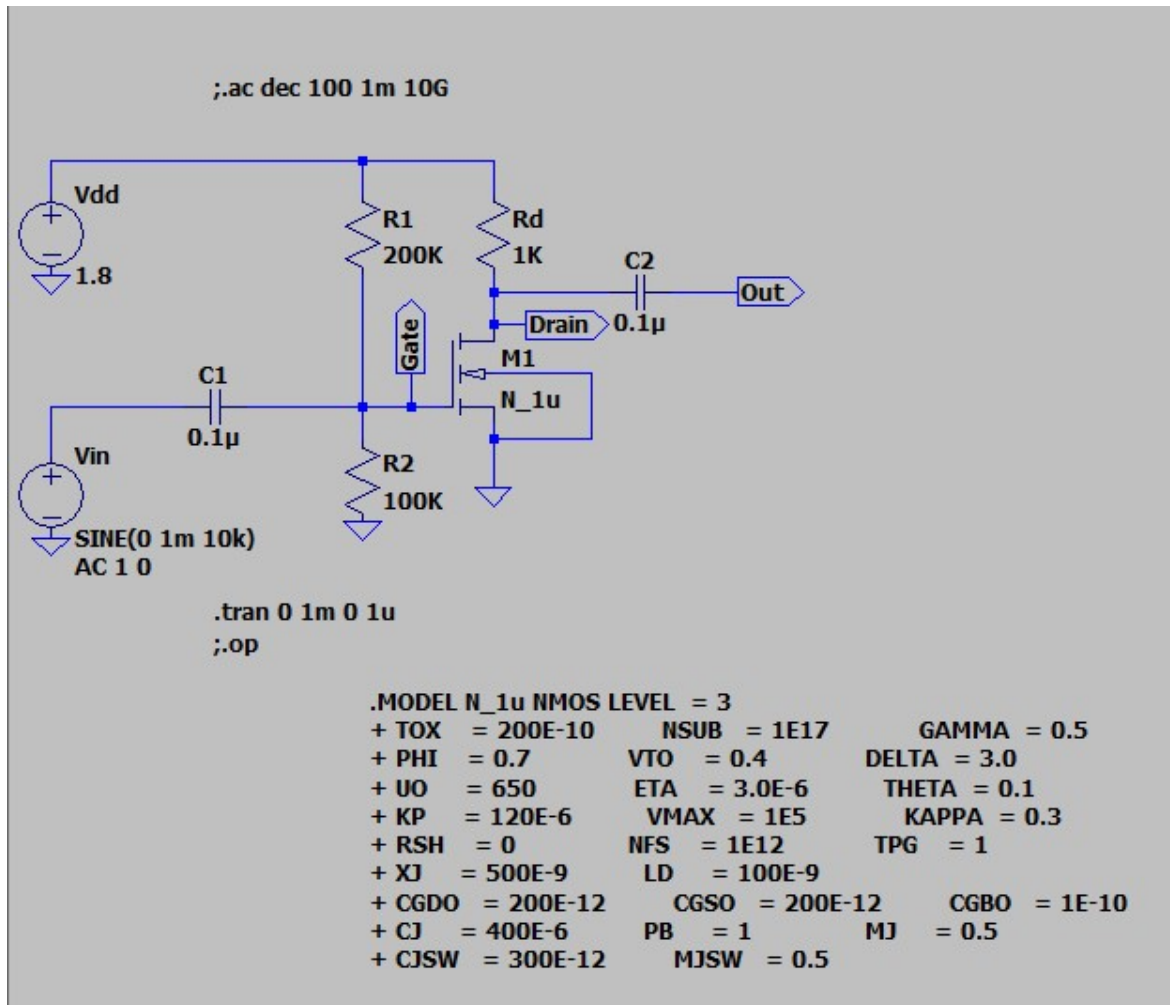


Output Waveforms:

DC operating Point


--- Operating Point ---

V(n001):	1.8	voltage
V(drain):	0.299922	voltage
V(gate):	0.6	voltage
V(n002):	0	voltage
V(out):	2.99922e-008	voltage
Id(M1):	0.00150011	device_current
Ig(M1):	0	device_current
Ib(M1):	-3.09921e-013	device_current
Is(M1):	-0.00150011	device_current
I(C1):	6e-020	device_current
I(C2):	-2.99922e-020	device_current
I(R2):	6e-006	device_current
I(R1):	6e-006	device_current
I(Rd):	0.00150008	device_current
I(Vdd):	-0.00150608	device_current
I(Vin):	6e-020	device_current

Transient characteristics

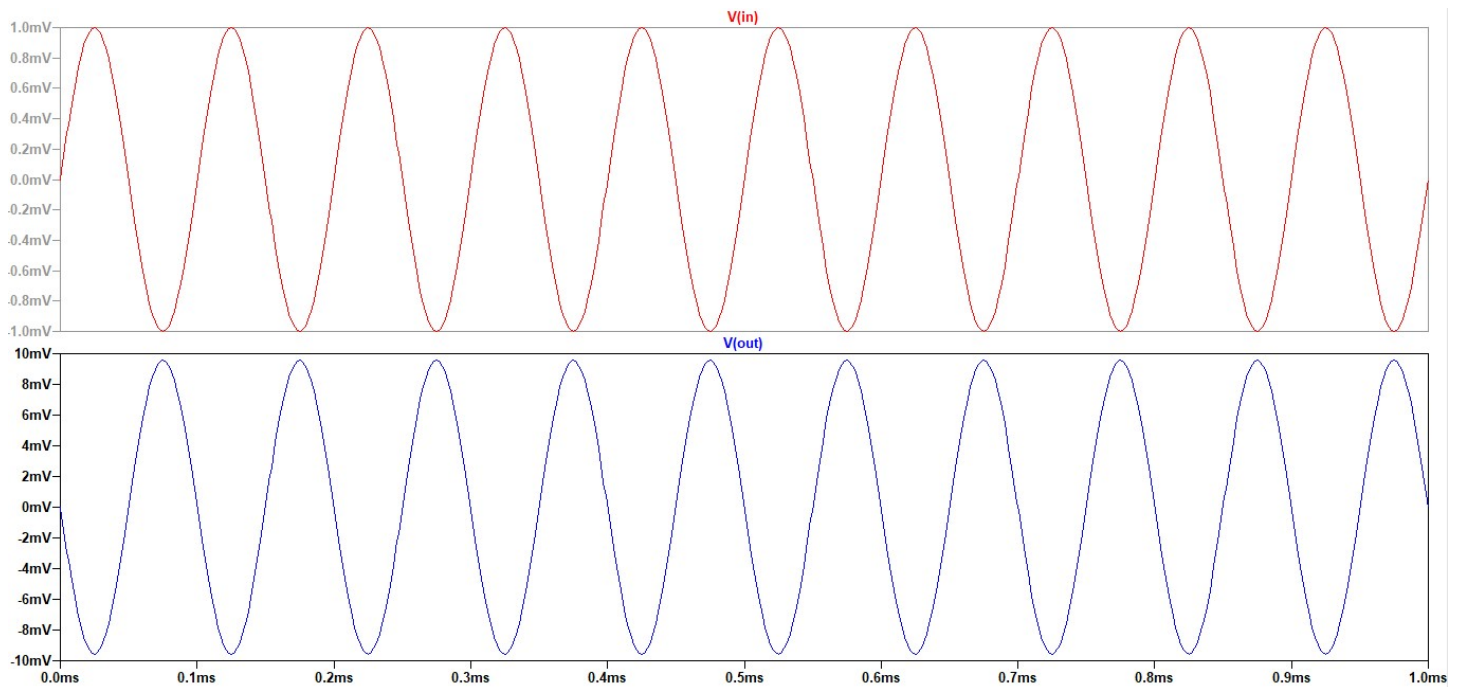

AC Analysis

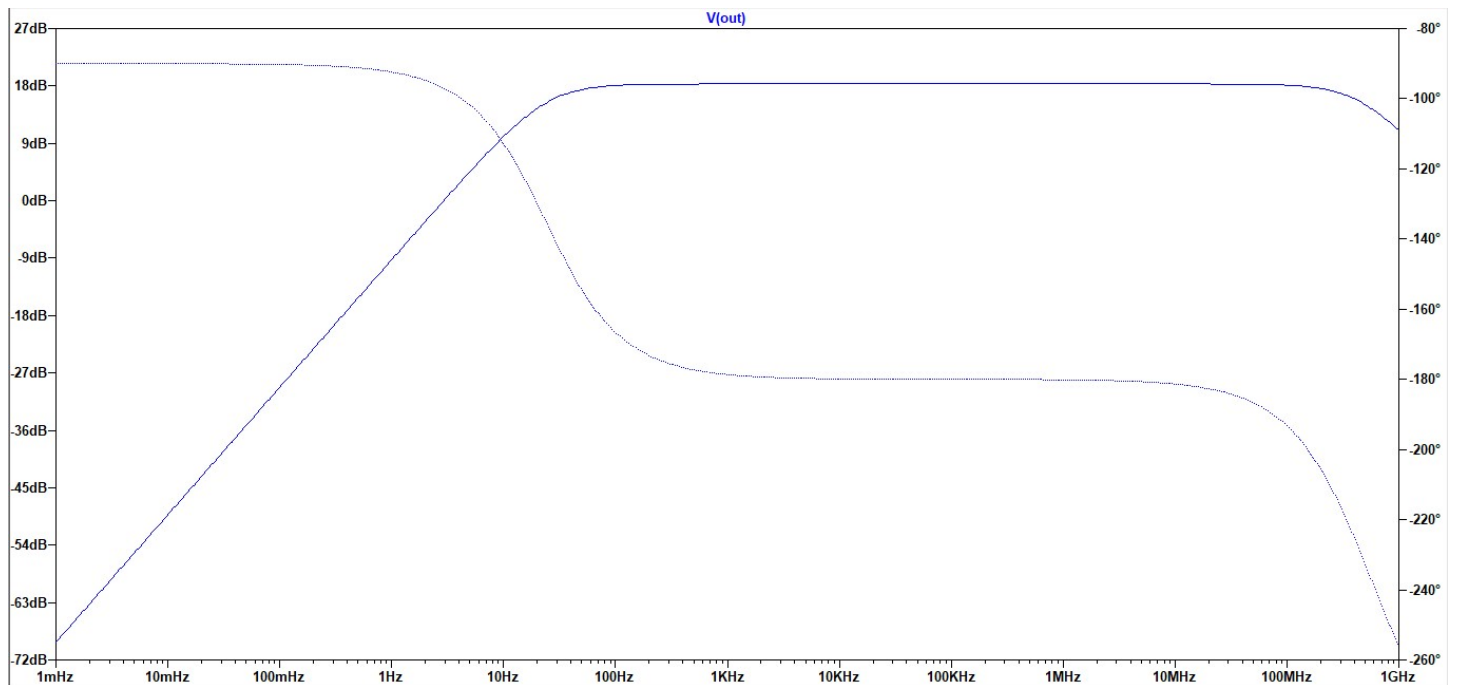

Result:

The circuit is designed for a gain of 10 and the output is verified to be correct. The transient and AC characteristics are visualized.