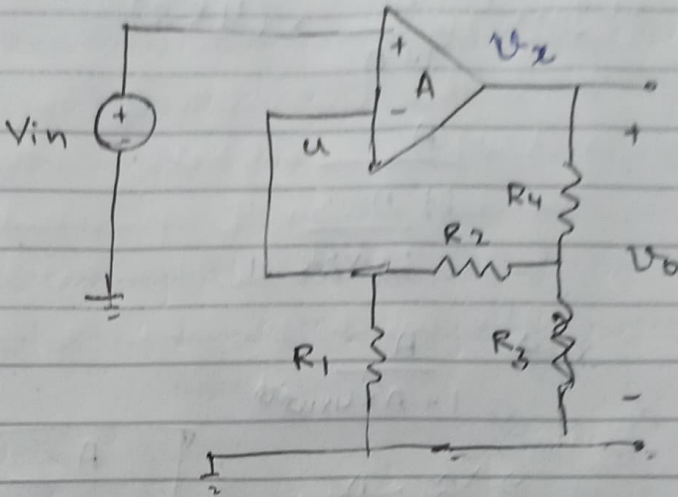


Assignment 4.

1. For the circuit shown below;



i) Find the expression for feedback factor k and closed loop voltage gain

$$V_x = (V_{in} - u) A$$

$$u = \frac{R_1 / (R_1 + R_2) \times \frac{R_3}{R_3 + R_4}}{1} + 1$$

$$2) \quad k = \frac{R_1 \times R_3}{(R_1 + R_2)(R_3 + R_4)}$$

$$CL \text{ gain} = \frac{A}{1 + A k} + 1$$

$$2) \quad \frac{A / \cancel{(R_1 + R_2)(R_3 + R_4)}}{\cancel{A R_1 R_3} + \cancel{(R_1 + R_2)(R_3 + R_4)}}$$

$$= \frac{A}{1 + A R_1 R_3 \over (R_1 + R_2)(R_3 + R_4)} + 1 //$$

ii) CL if $R_1 = R_2 = R_3 = R_4 = 1k\Omega$

$$1) C_{Lgain} = \frac{A}{1+A} \times (4k\Omega)$$

$$= \frac{A}{1+A} \times \frac{2k \times 2k\Omega}{4}$$

$$2) \frac{A}{1+A \times 4k\Omega}$$

$$\rightarrow \approx A_{11}$$

$$= \boxed{\frac{A}{1+A/4}} + 1$$

iii) if $A = 200 V/V$

$$C_{Lgain} = \frac{200}{1+200 \times \frac{4k\Omega}{4}}$$

$$= \frac{200}{1+800} \times \frac{200}{4}$$

$$= \frac{200}{1+800} \times 50$$

$$\approx \frac{200}{801} \times 50 \approx 4+1 \approx 5$$

$$\frac{A}{1+A} = 0.2$$

$$K = 0.2$$

3. Write a short note on slew rate, PSRR and Offset effects in opamps.

Slew rate:

The slew rate of an electronic circuit is defined as the rate of change of the voltage per unit time. Slew rate is usually expressed in units of $V/\mu s$.

$$SR = \max \left| \frac{dv_{out}(t)}{dt} \right|$$

where $v_{out}(t)$ is the output produced by the amplifier as a function of time t .

PSRR:

Power Supply Rejection Ratio (PSRR) can be referred either to the output (RTO) or the input (RTI). The RTI value can be obtained by dividing the RTO value by the amplifier gain. In the case of the traditional op-amp, this would be the noise gain. ~~the~~
data sheet

OFFSET:

May be due to error occurred during fabrication and finite gain of the opamp. It is due to the inherent mismatch of the input transistors and components during fabrication.

4. Write a short note on noise bandwidth & Noise figure.

Noise bandwidth:

It is the bandwidth of an ideal rectangular amplifier. In other words the definition of equivalent noise bandwidth is the bandwidth of a noise filter which produces the same noise.

Noise figure:

It is used to indicate the quality of amplifier. There are various methods used to measure noise figure.

i) Gain Method

ii) Y factor method.

iii) Noise figure meter method.

